

# Power Supply and automatic Voltage Control

12-09-13

**steag**

# **Understanding ESP Controls**

## Power Supply System

- The power supply system is designed to provide voltage to the electrical field (or bus section) at the highest possible level.
  - The voltage must be controlled to avoid causing sustained arcing or sparking between the electrodes and the collecting plates.
  - [Precipitator power system](#) animated schematic showing representative components.
- 
- When electrical fields are in series, the power supply for each field can be adjusted to optimize operation of that field.
  - Likewise, having more than one electrical bus section in parallel allows adjustments to compensate for their differences, so that power input can be optimized.

# Components

The power supply system has four basic components:

- Automatic voltage control
- Step-up transformer
- High-voltage rectifier
- Sensing device
- Voltage control

## Automatic voltage control

- a. varies the power to the transformer-rectifier
- b. in response to signals received from sensors in the precipitator and the transformer-rectifier itself.
- c. monitors the electrical conditions inside the precipitator,
- d. protects the internal components from arc-over damages, and
- e. protects the transformer-rectifier and other components in the primary circuit.

## AVC Contd....

- The ideal automatic voltage control would produce
- a. maximum collecting efficiency by holding the operating voltage of the precipitator at a level just below the spark-over voltage.
  - b. this level cannot be achieved given that conditions change from moment to moment.
  - c. Instead, the automatic voltage control increases output from the transformer-rectifier until a spark occurs.
  - d. Then the control resets to a lower power level, and the power increases again until the next spark occurs.

## **Automatic Voltage Controllers** (for Electrostatic Precipitators)

An electronic device used to control the application of D.C. power into a field of an electrostatic precipitator.

### **Functions:**

- *Optimize power application*:- to deliver as much useful electrical power to the corresponding field(s) as possible.
- *Spark reaction* – When the voltage applied to the field is too high for the conditions at the time, a spark over (or corona discharge) will occur.

Detrimentially high amounts of current can occur during a spark over if not properly controlled, which could damage the fields.

A voltage controller will monitor the primary and secondary voltage and current of the circuit, and detect a spark over condition.

Once detected, the power applied to the field will be immediately cut off or reduced, which will stop the spark.

After a short amount of time the power will be ramped back up, and the process will start over.


- *Protect system components by adhering to component limitations* – The Transformer Rectifier set (TR set) can be damaged by excessive amounts of current or voltage flowing through it.
- Each TR set has voltage and current limits established by the manufacturer, which are labeled on an attached nameplate.
- These nameplate limit values (typically primary and secondary current, and voltage) are programmed into the voltage controller.
- *Tripping* – When a condition occurs that the voltage controller cannot control, often times the voltage controller will trip.
- A trip means the voltage controller (by way of the contactor) will shut off the individual precipitator power circuit.
- A short inside the electrostatic precipitator field caused by a fallen discharge electrode (wire), or a shorted out Silicone Controlled Rectifier are examples of conditions that a voltage controller cannot control.




# Efficiency vs. Specific Corona Power




KNOW WHERE YOUR ESP RUNS ON THE CURVE

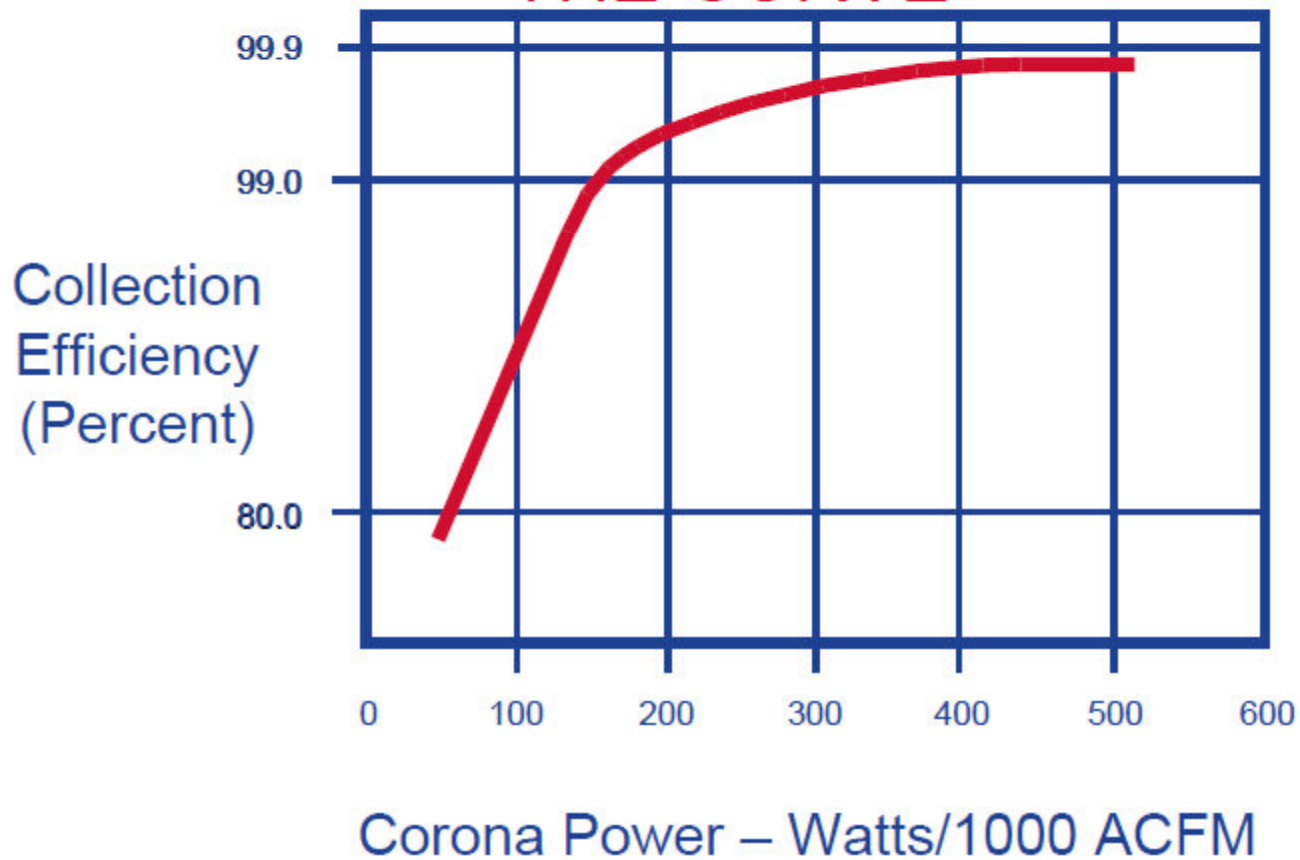

# AVC Cabinet, CLR & T/R Set

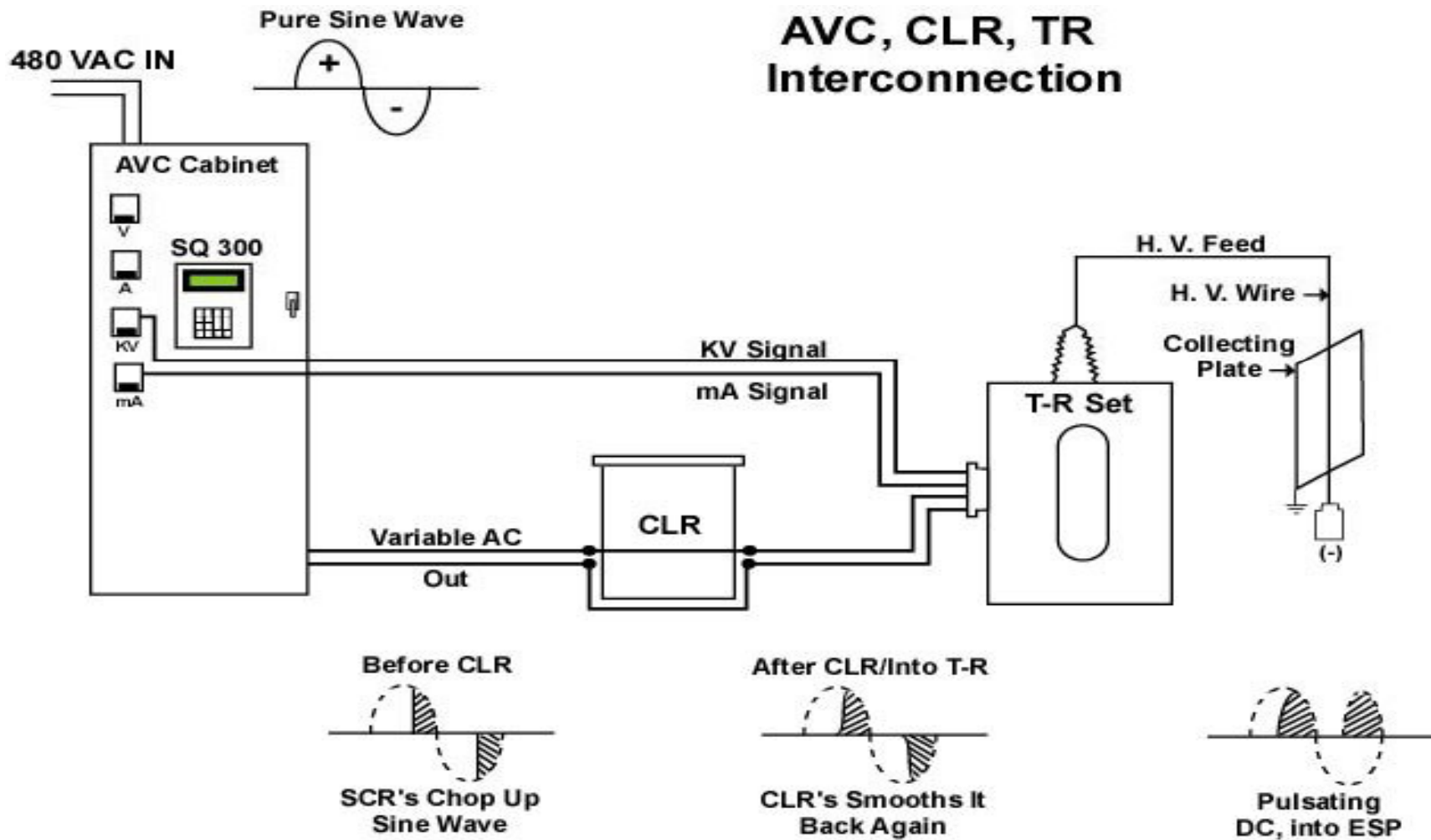

# Typical SCR-CLR Electrical System

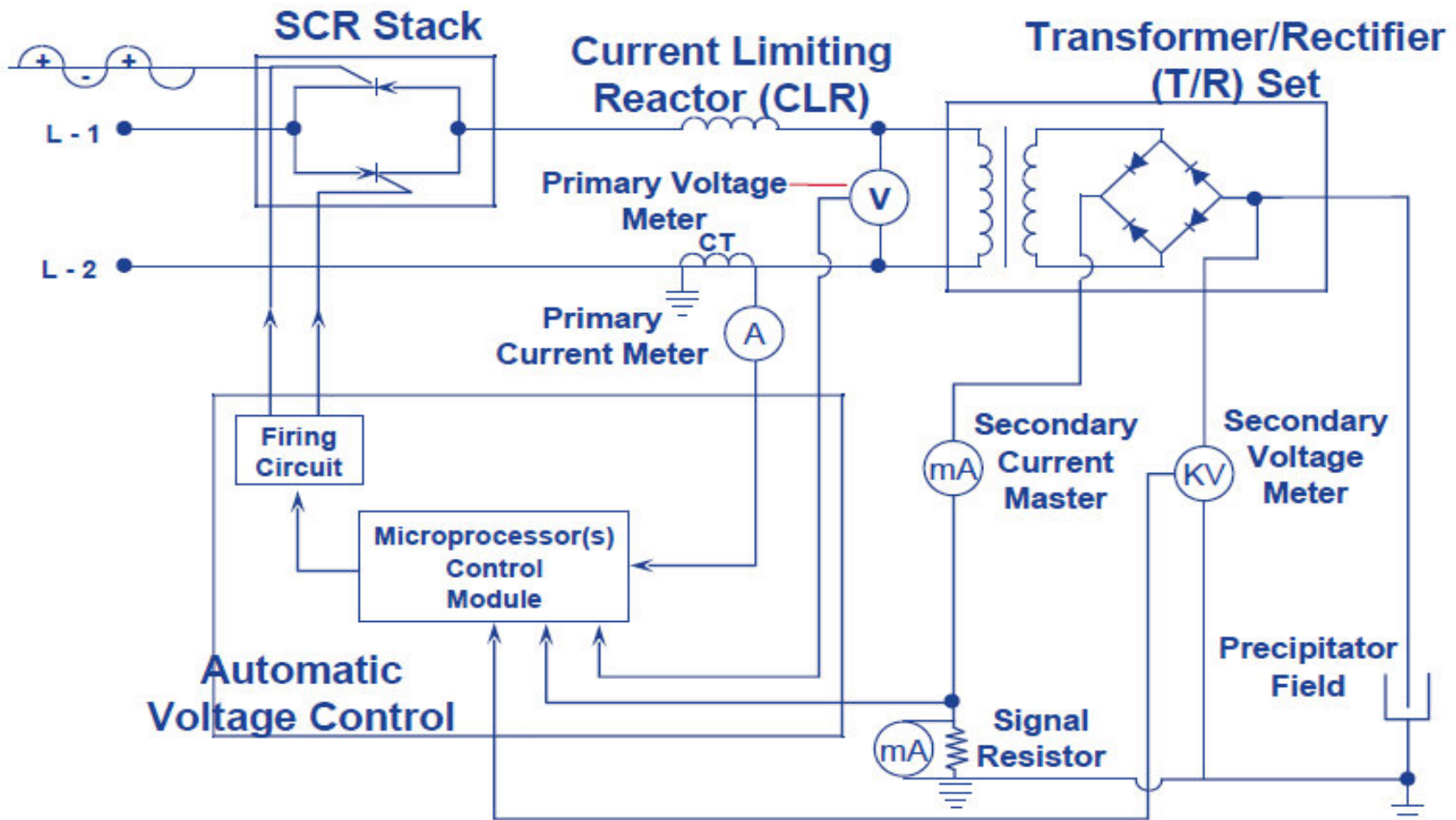

## Typical SCR-CLR Electrical System

steag

**Just Remember, the Primary of a T-R Set is Rated in Units of RMS, the Secondary is in Average**

- 400 V AC RMS
- 120 A AC RMS
- 45 KV DC Average
- 750 mA DC Average

**Therefore use an RMS Reading Meter to Calibrate the Primary Meters**

# How to Tell The Difference?



Iron Vane  
Movement




D'Arsonval  
Average

RMS

**The Meter Scale Distance is not the Same on the RMS  
Meter**

# Primary Current Meter

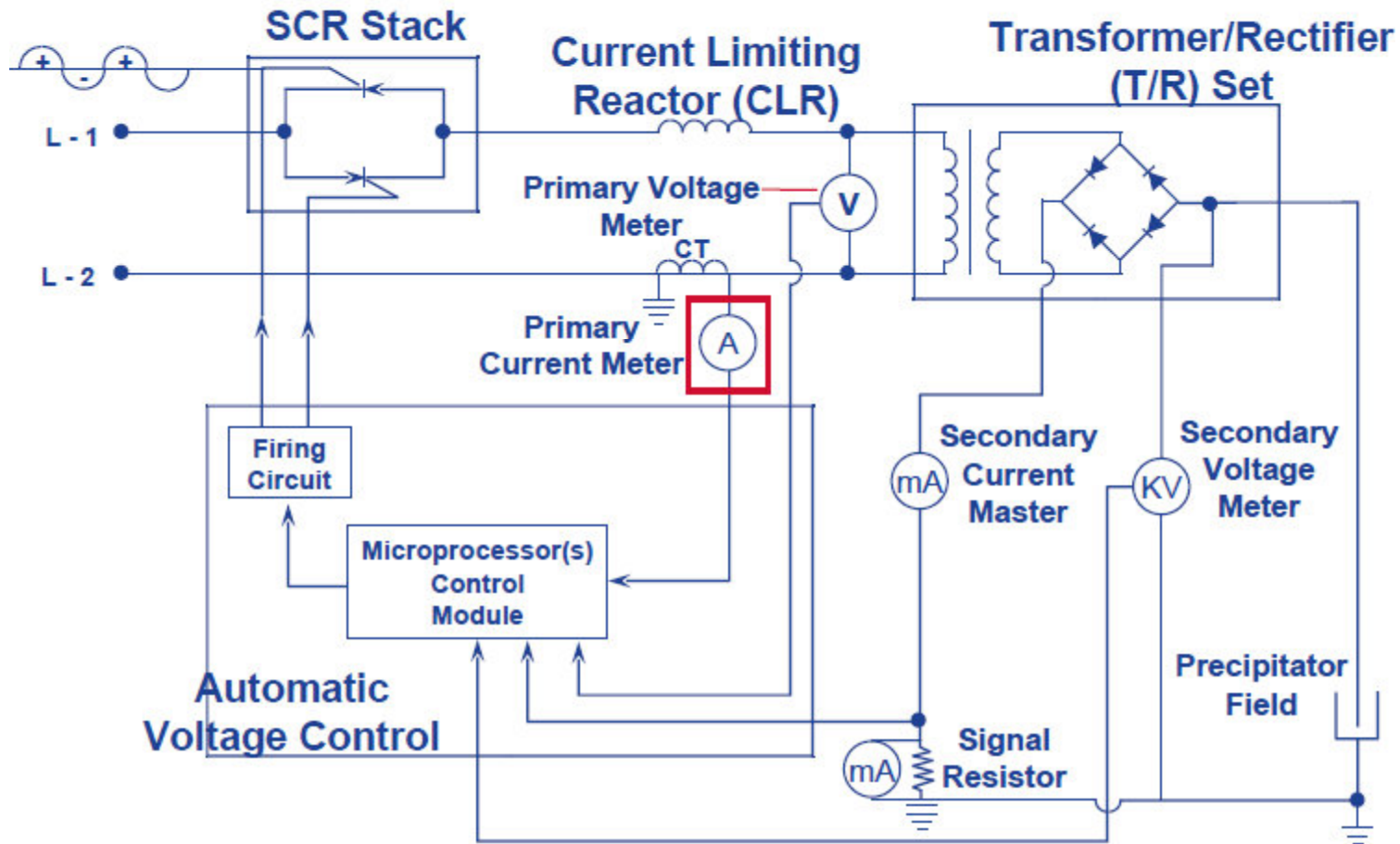


# Finding the Primary Current Waveform

steag




# Primary Current – A Chopped Sine Wave

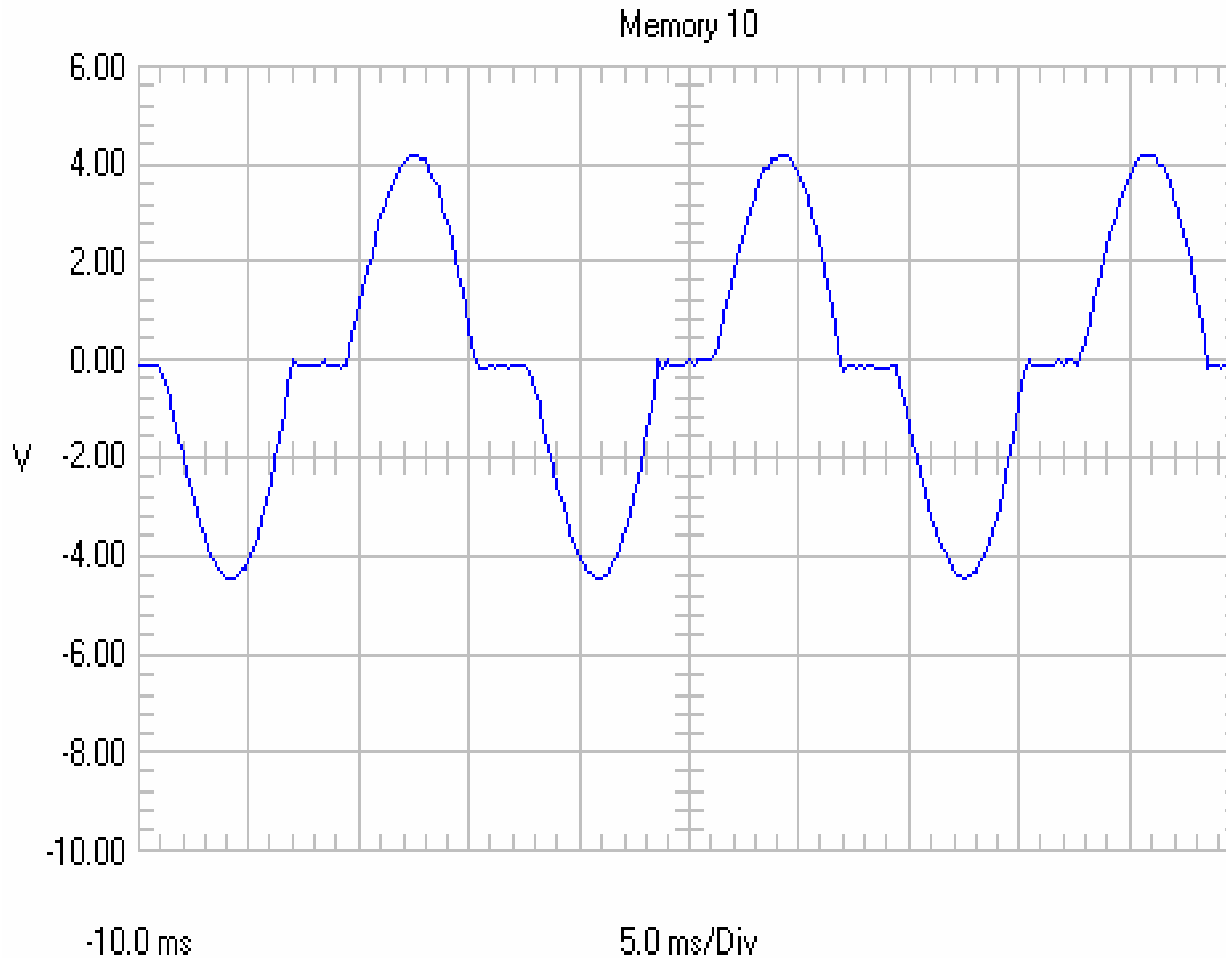


Datablock	
Name	= Memory 10
Date	= 12/4/97
Time	= 3:16:25 PM
Y Scale	= 2.00 V/Div
Y At 50%	= -2.00 V
X Scale	= 5.0 ms/Div
X At 0%	= -10.0 ms
X Size	= 250 (512)
Maximum	= 4.24 V
Minimum	= -4.48 V


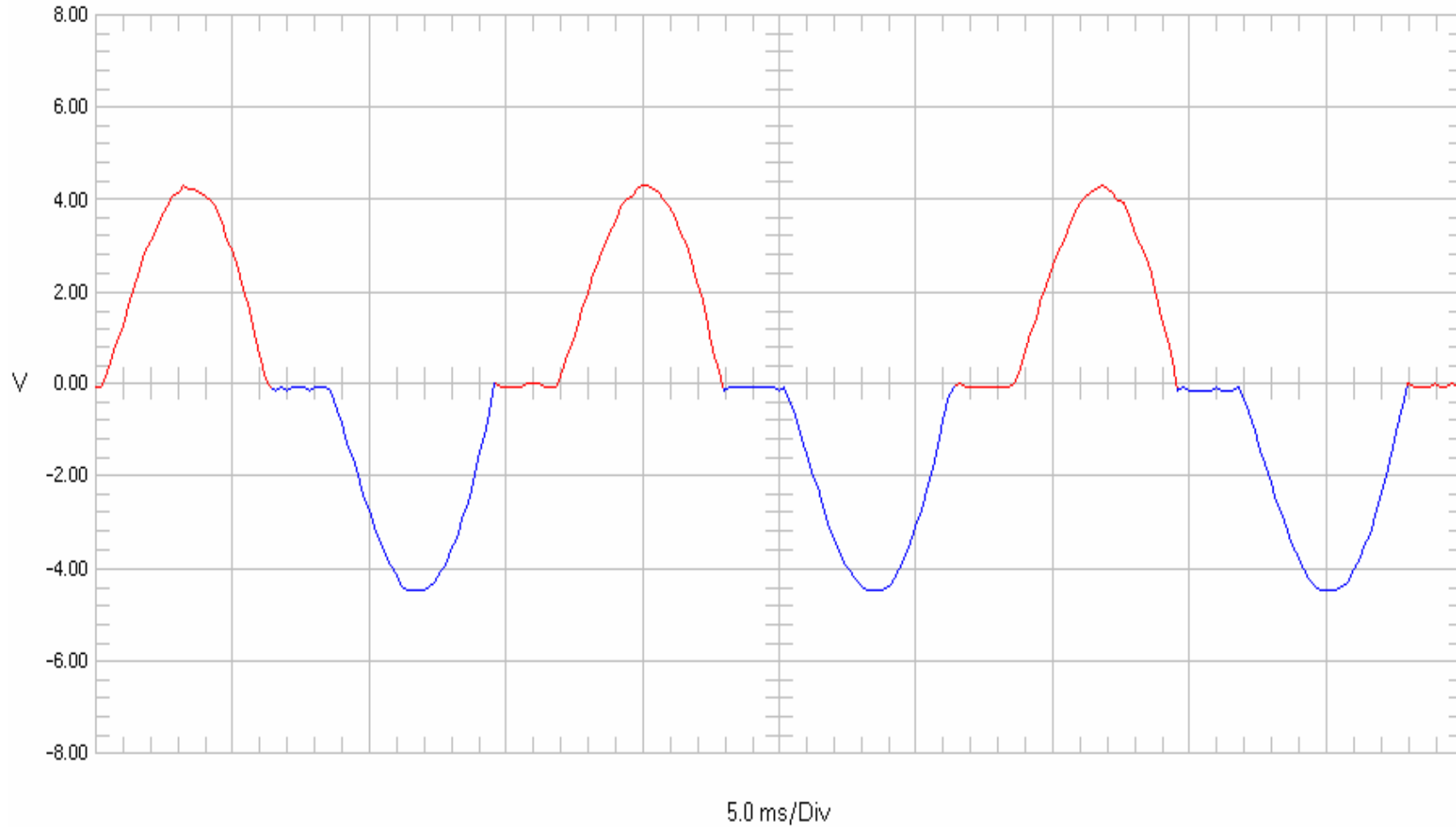
# Primary Current Waveform - Positive and Negative Half-Cycles = SCR 1 and SCR 2




# Secondary Current Meter

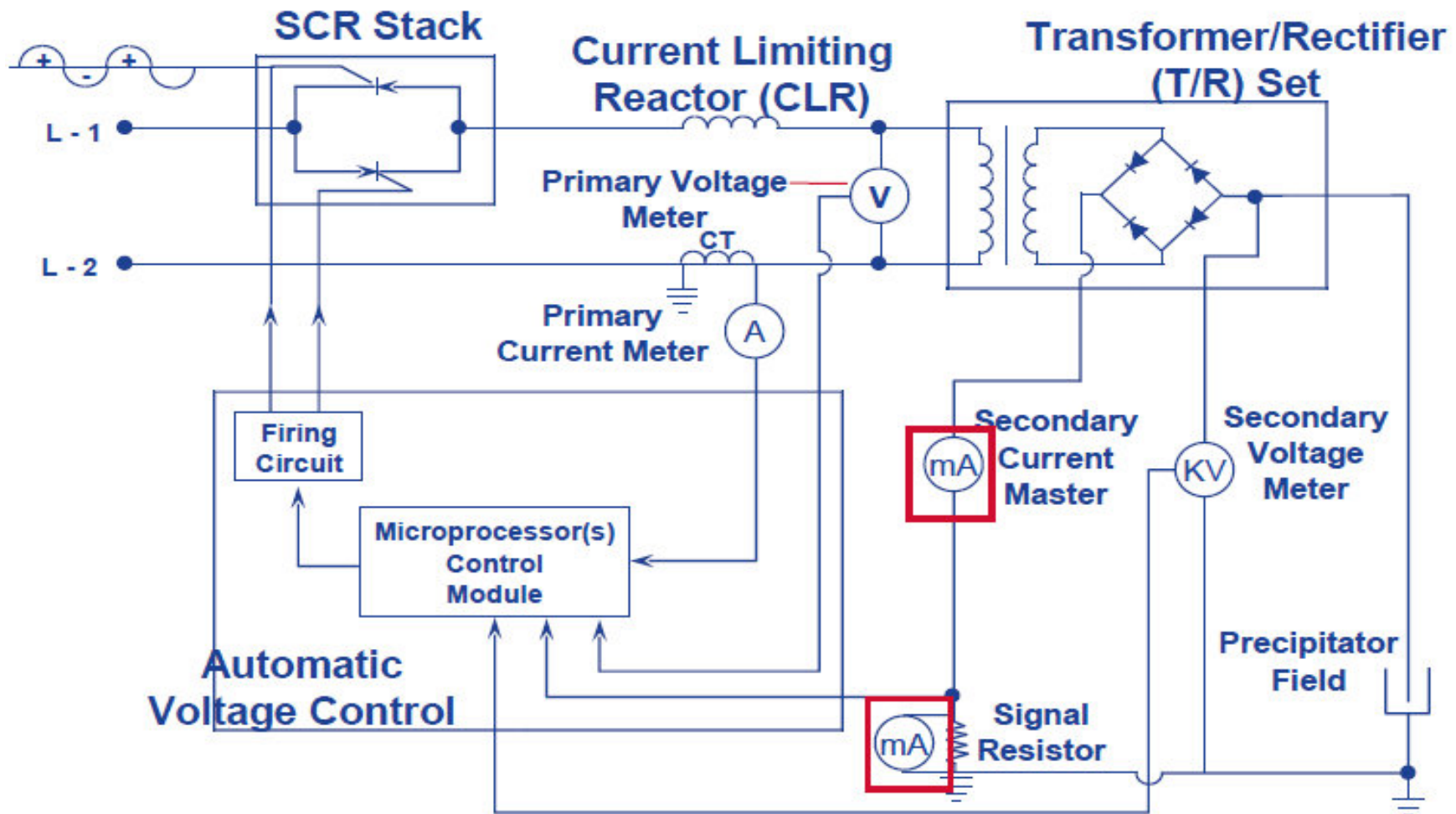


## Finding the mA Signal

steag

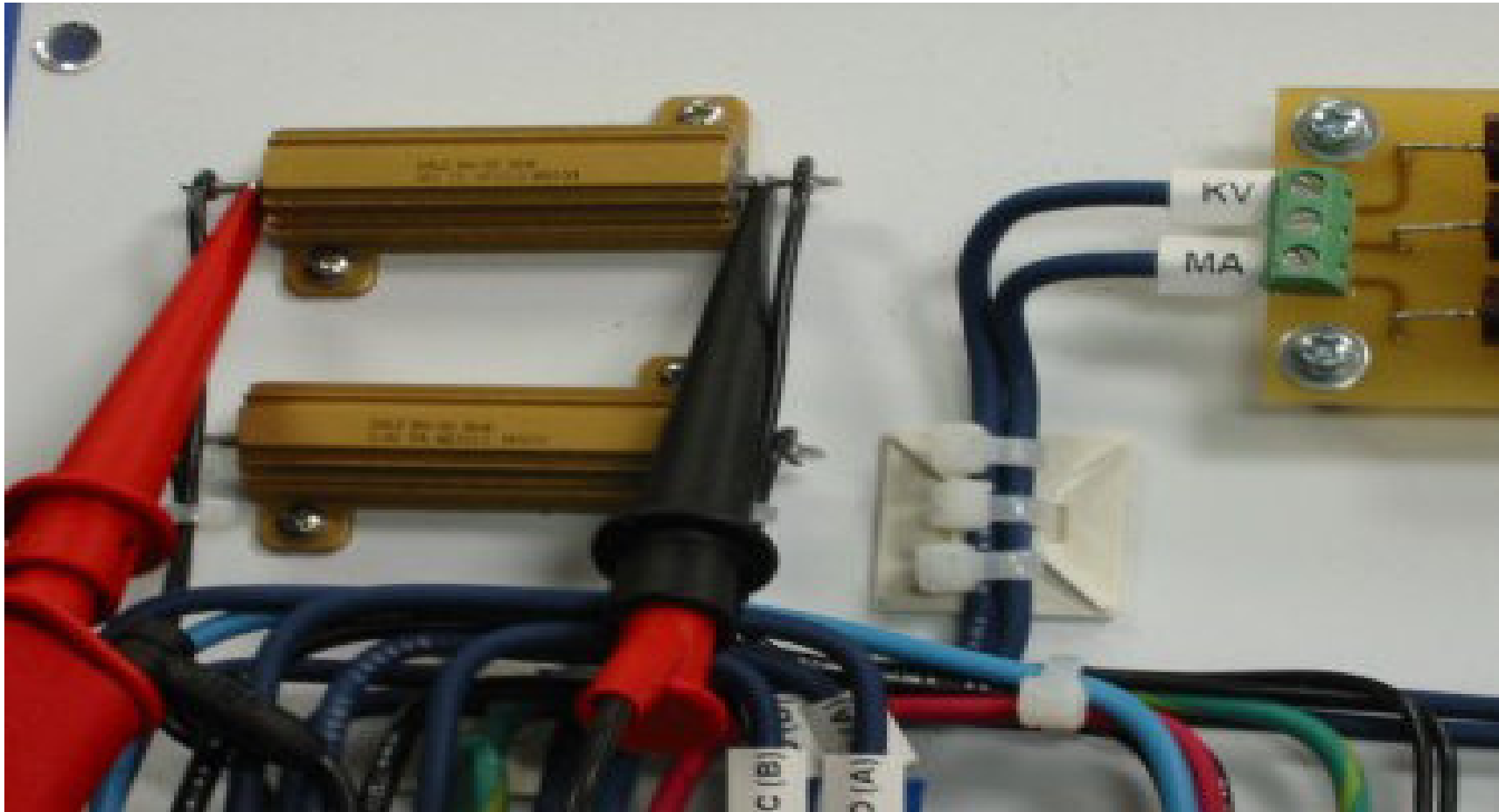


## Secondary Current – Pulsating DC

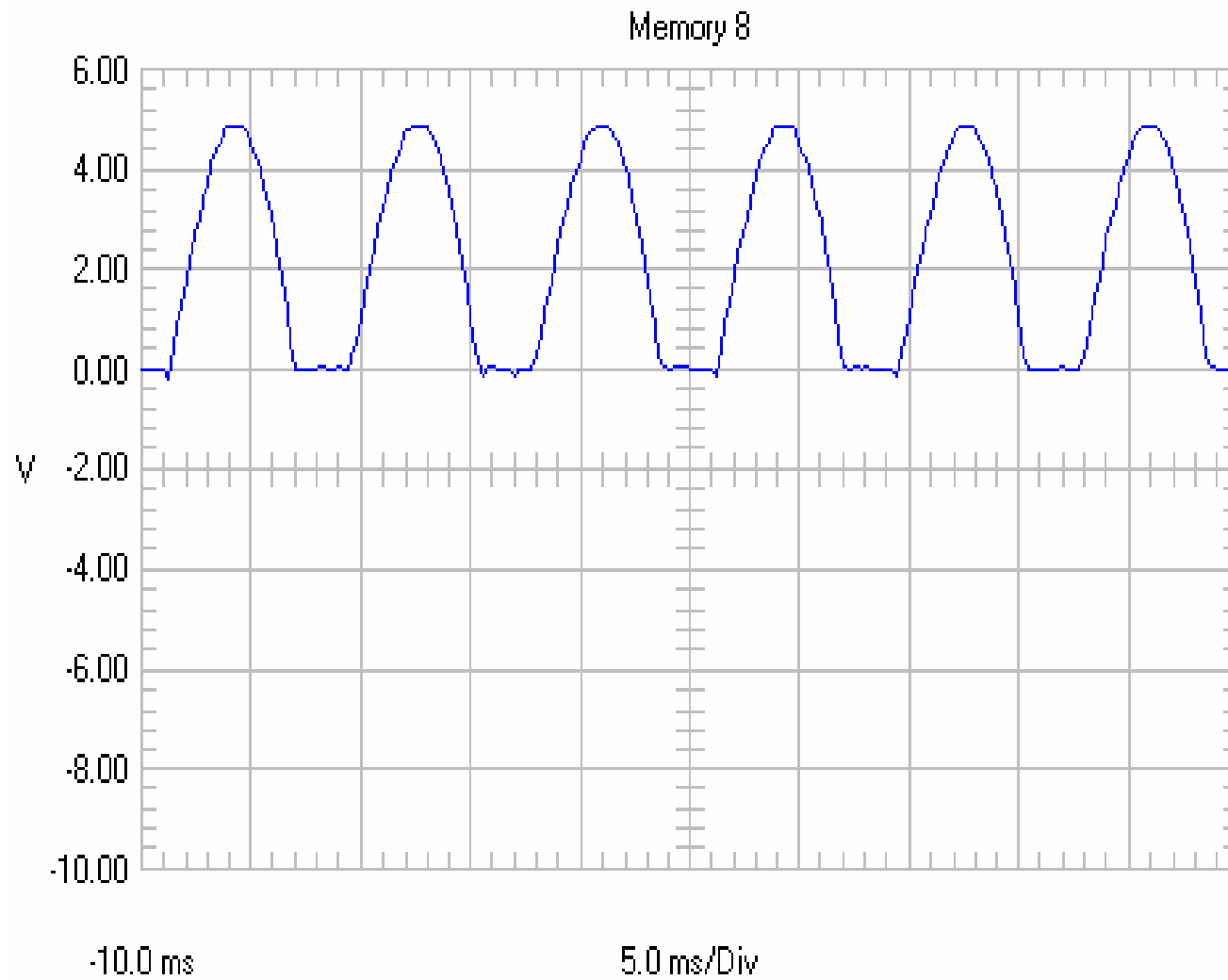

Datablock	
Name	= Memory 8
Date	= 12/4/97
Time	= 3:16:23 PM
Y Scale	= 2.00 V/Div
Y At 50%	= -2.00 V
X Scale	= 5.0 ms/Div
X At 0%	= -10.0 ms
X Size	= 250 (512)
Maximum	= 4.88 V
Minimum	= -0.16 V

# Typical Primary and Secondary current

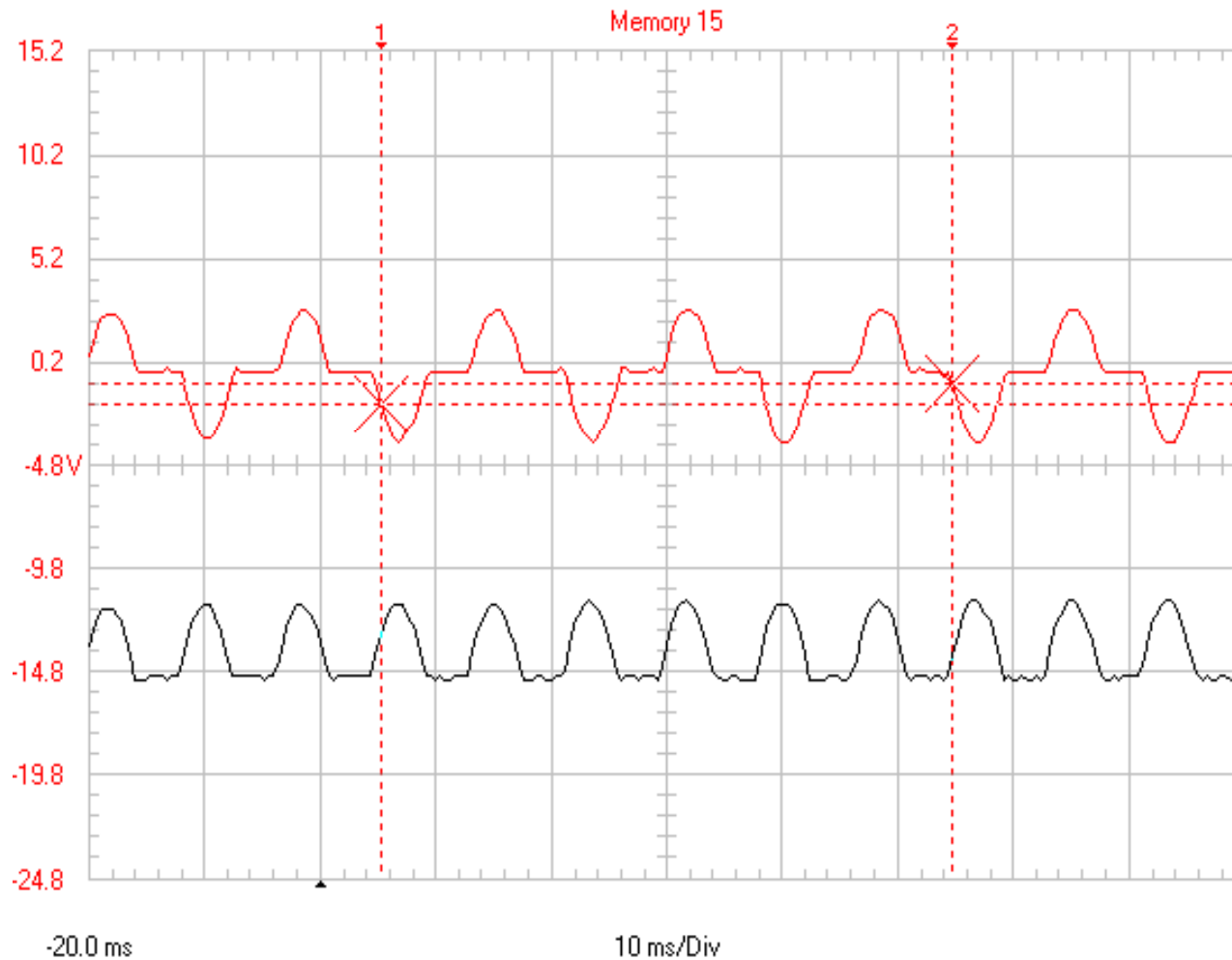


Datablock		
Name	= Memory 15	Memory 16
Date	= 12/4/2003	12/4/2003
Time	= 6:07:44 PM	6:07:44 PM
Y Scale	= 5 V/Div	5 V/Div
Y At 50%	= -4.8 V	10.0 V
X Scale	= 10 ms/Div	10 ms/Div
X At 0%	= -20.0 ms	-20.0 ms
X Size	= 250 (512)	250 (512)
Maximum	= 3.0 V	3.6 V
Minimum	= -3.8 V	-0.4 V


Cursor Values	
X1:	5.2 ms
X2:	54.8 ms
dX:	49.6 ms
Y1:	-1.8 V
Y2:	-0.8 V
dY:	1.0 V

11&12C Pri/Sec

# Secondary Voltage Meter

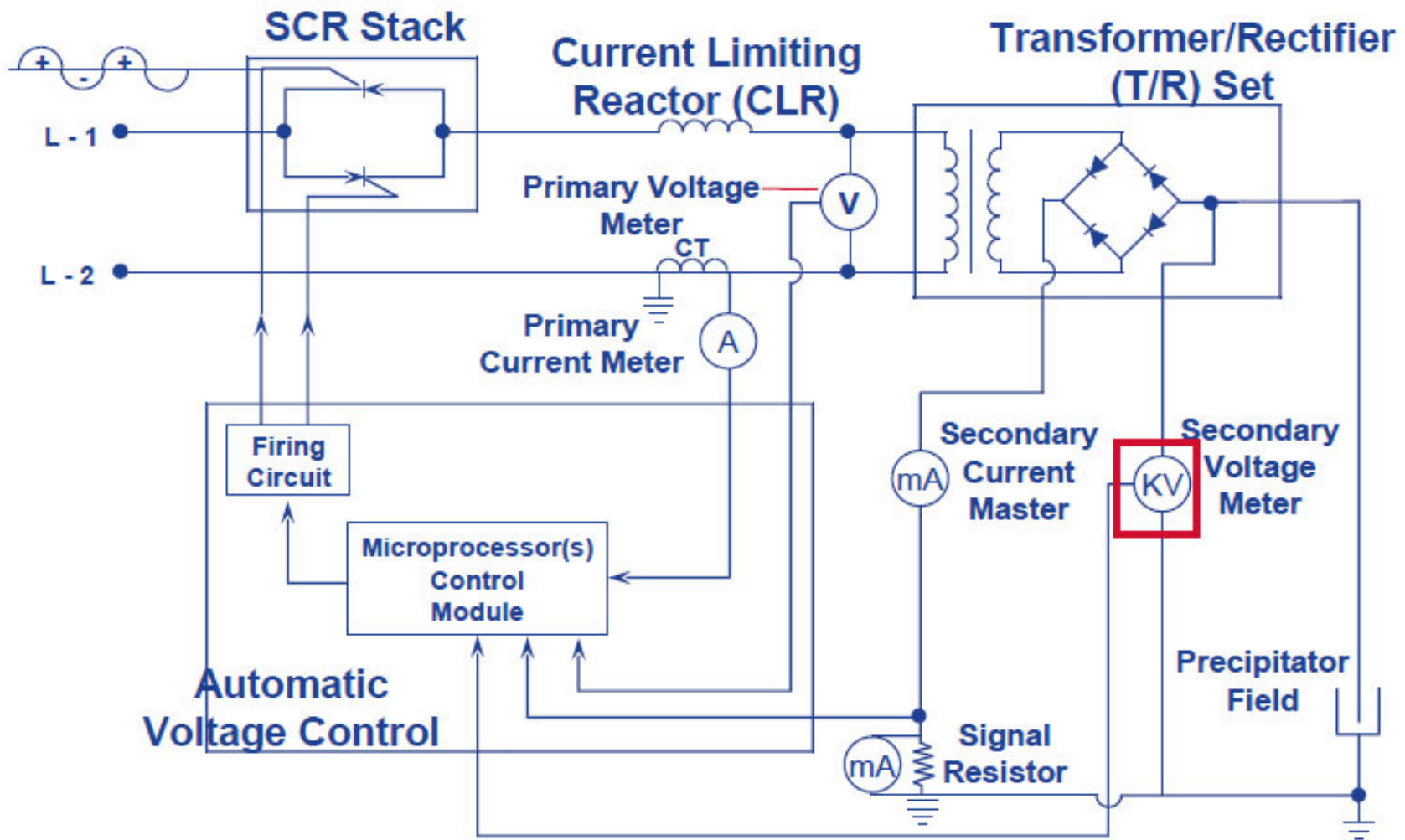

# Current Limit - mA & KV

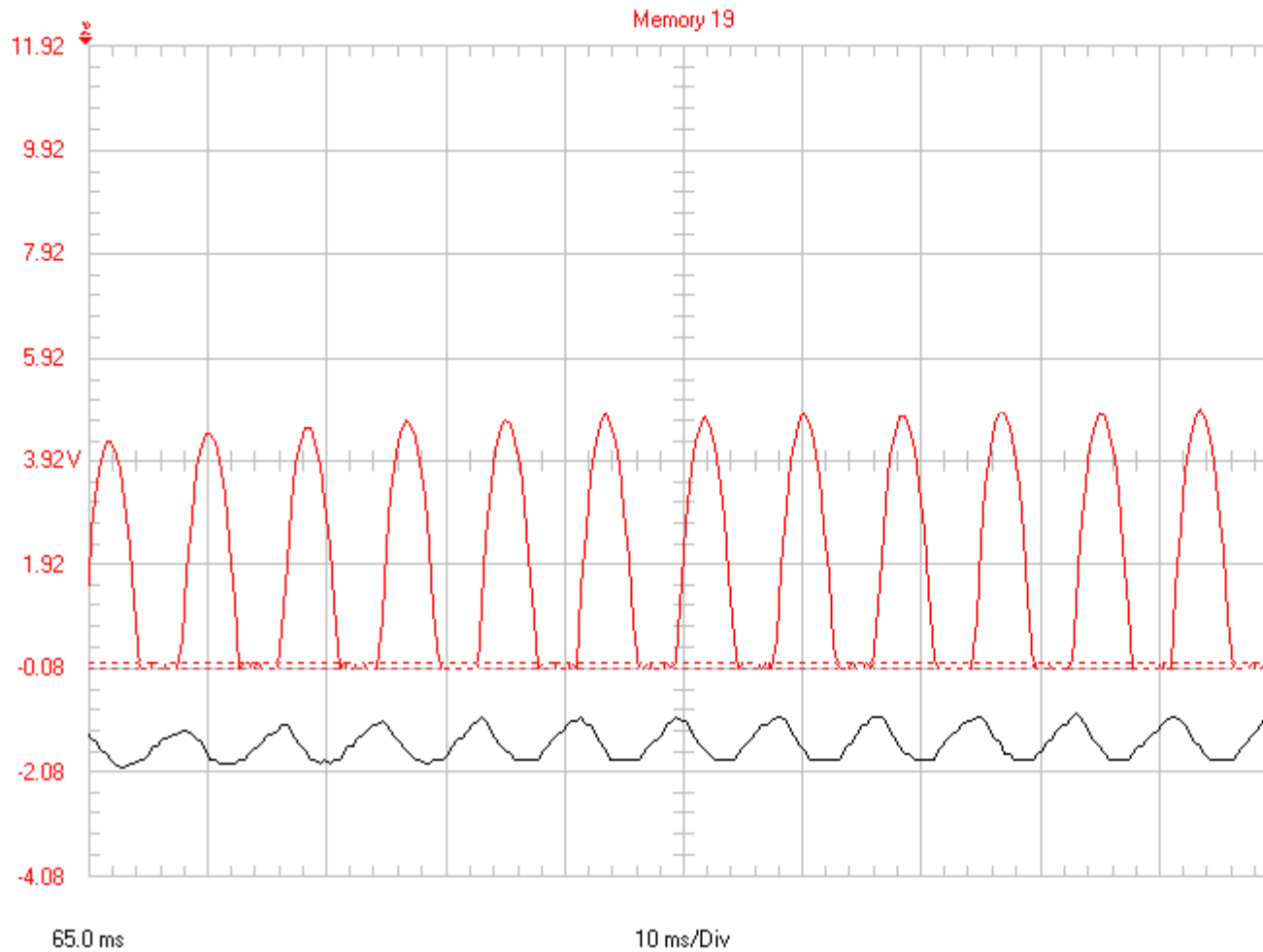


Datablock		
Name	= Memory 19	Memory 20
Date	= 12/1/2003	12/1/2003
Time	= 4:16:05 PM	4:16:05 PM
Y Scale	= 2 V/Div	2 V/Div
Y At 50%	= 3.92 V	4.00 V
X Scale	= 10 ms/Div	10 ms/Div
X At 0%	= 65.0 ms	65.0 ms
X Size	= 250 (512)	250 (512)
Maximum	= 9.28 V	-0.08 V
Minimum	= -0.08 V	-1.92 V

Cursor Values	
X1:	5.2 ms
X2:	54.8 ms
dX:	49.6 ms
Y1:	-0.08 V
Y2:	0.00 V
dY:	0.08 V


9&10F mA/KV
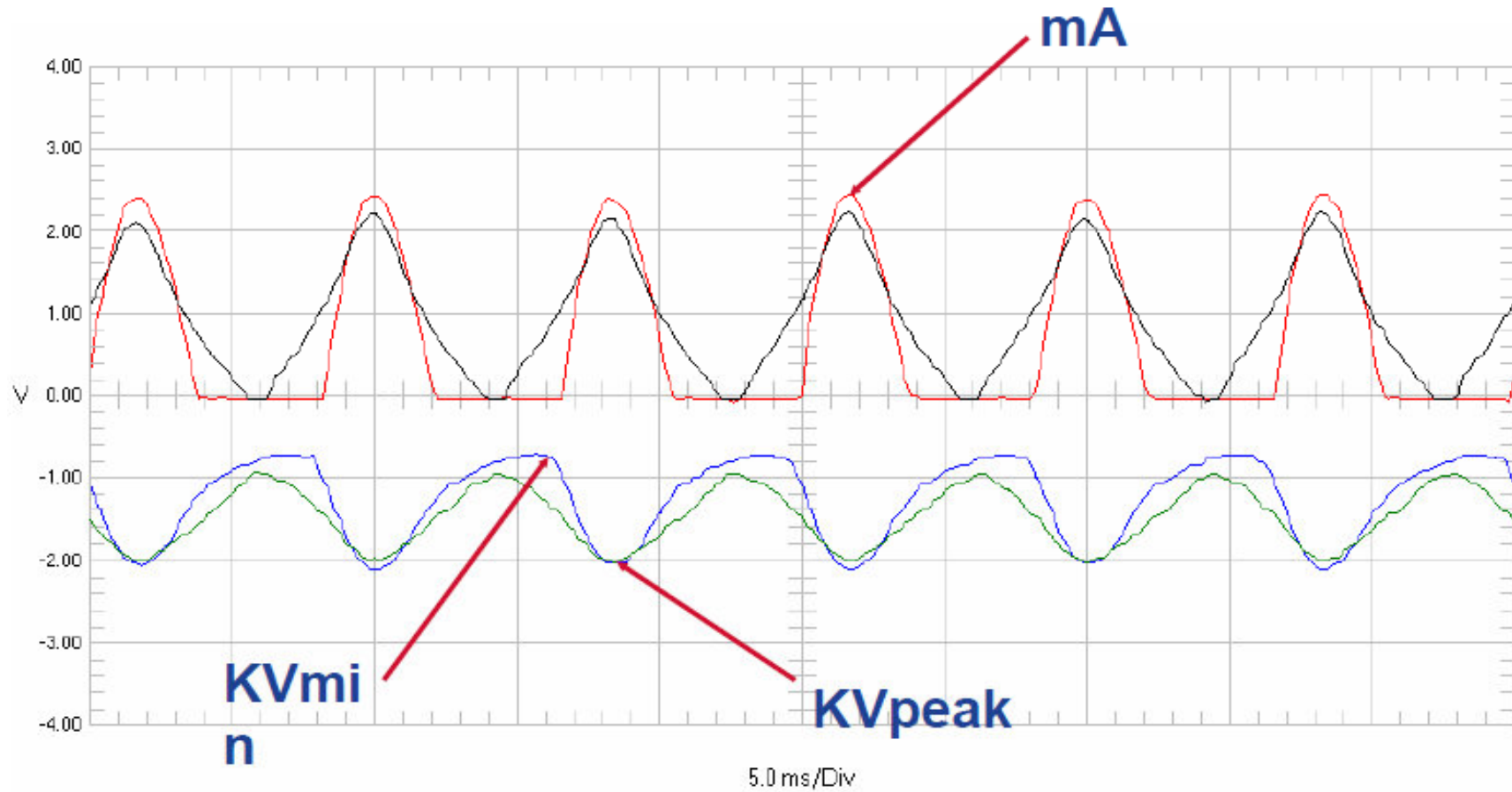
# Secondary Voltage Waveforms – True Negative






# Next – The Automatic Voltage Control

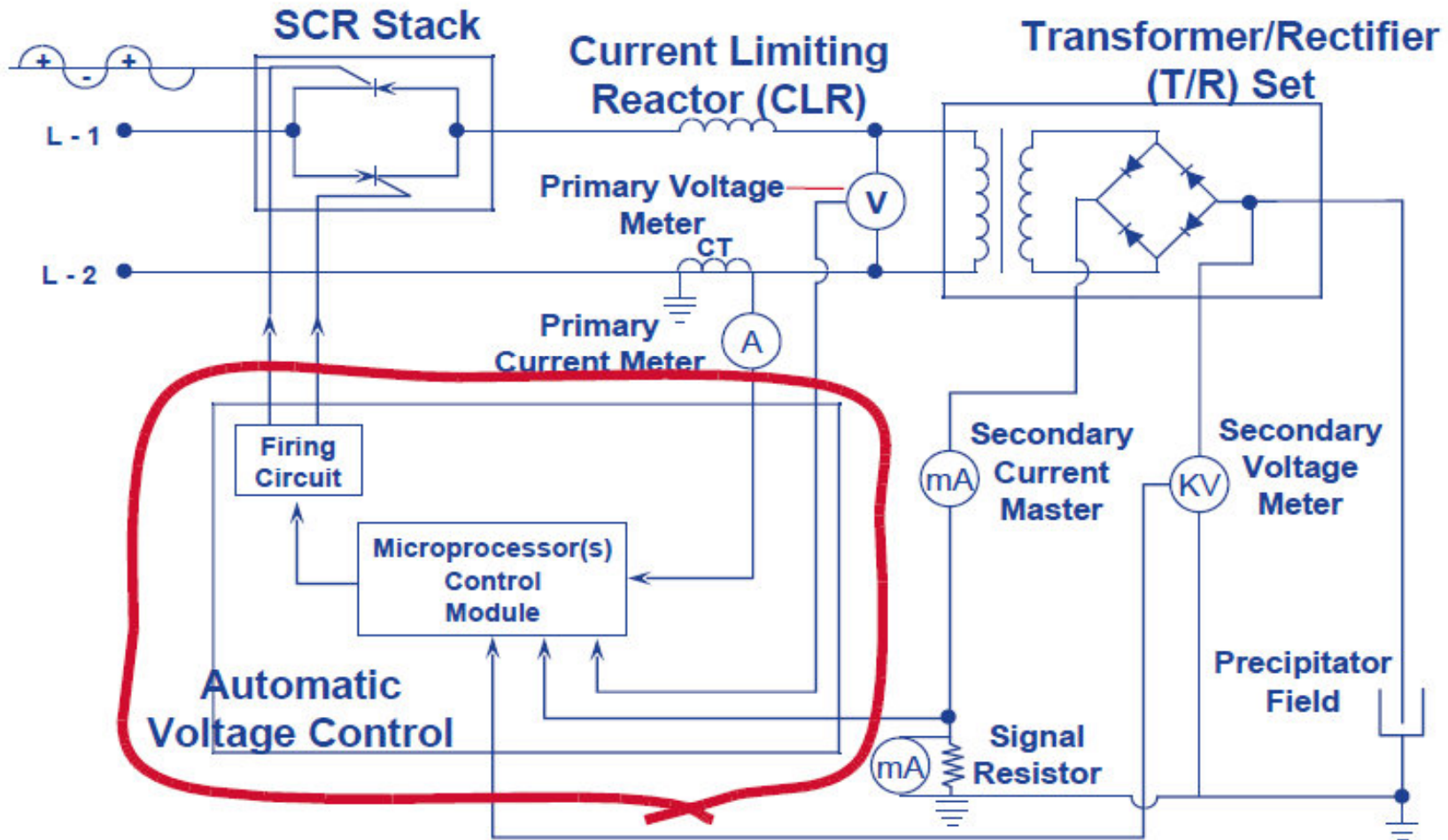

**The AVC  
is the BRAIN  
of the ESP**

## Older Analog AVC

steag

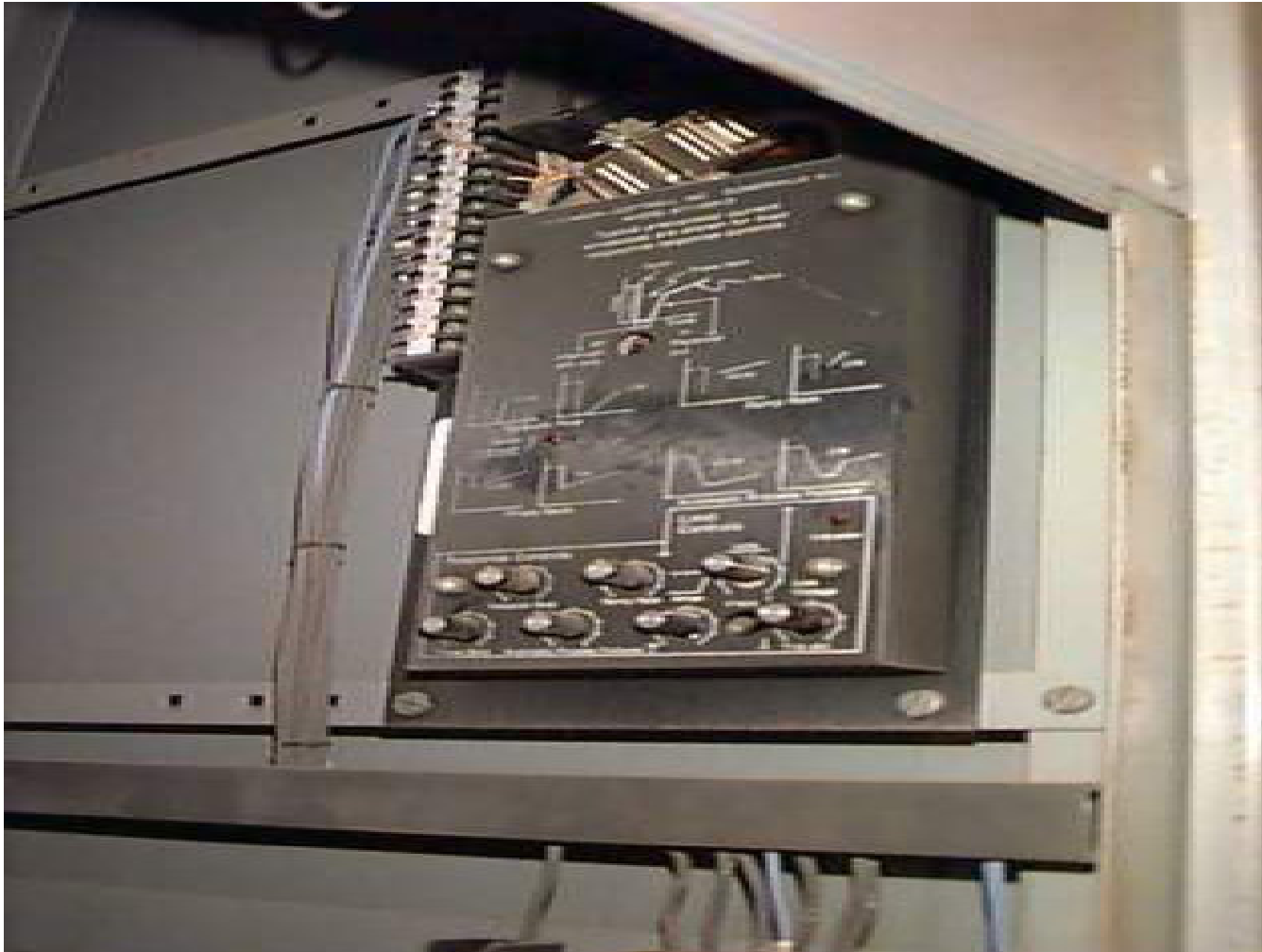

# Microprocessor Based AVC

steag



## The AVC has 2 Jobs to Execute



- **Control the amount of sparking in the ESP.**
- **If a T/R set is not sparking, then its AVC should be pushing that T/R set to one of its pre-set, healthy limits (volts, amps, KV, mA, or firing angle).**


## The AVC feedback?




But how does the AVC know  
what's happening in the  
ESP?

The mA signal is its eyes!

Transformer Rectifier Set

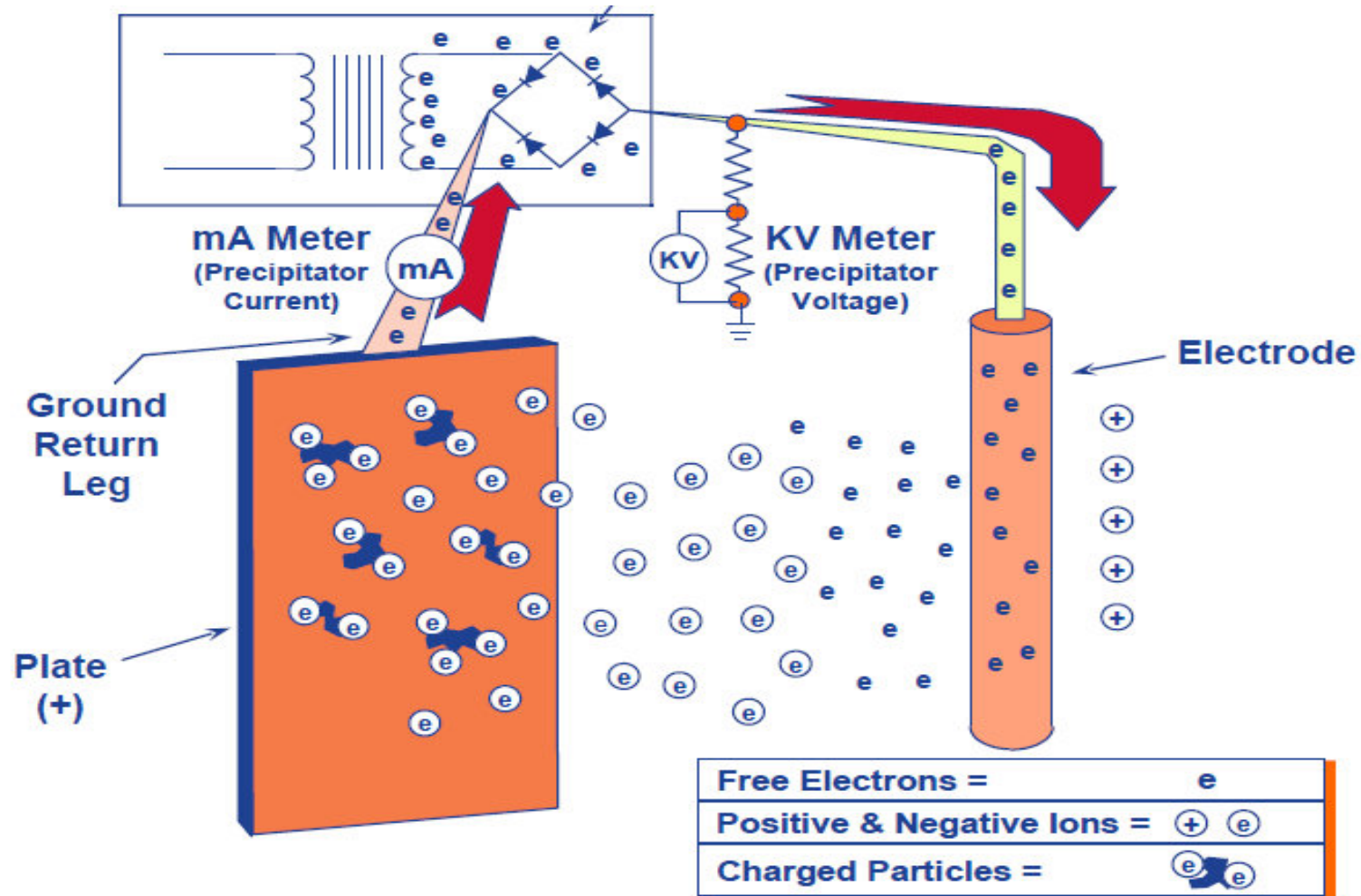


# AVC Cabinet, CLR & T/R Set

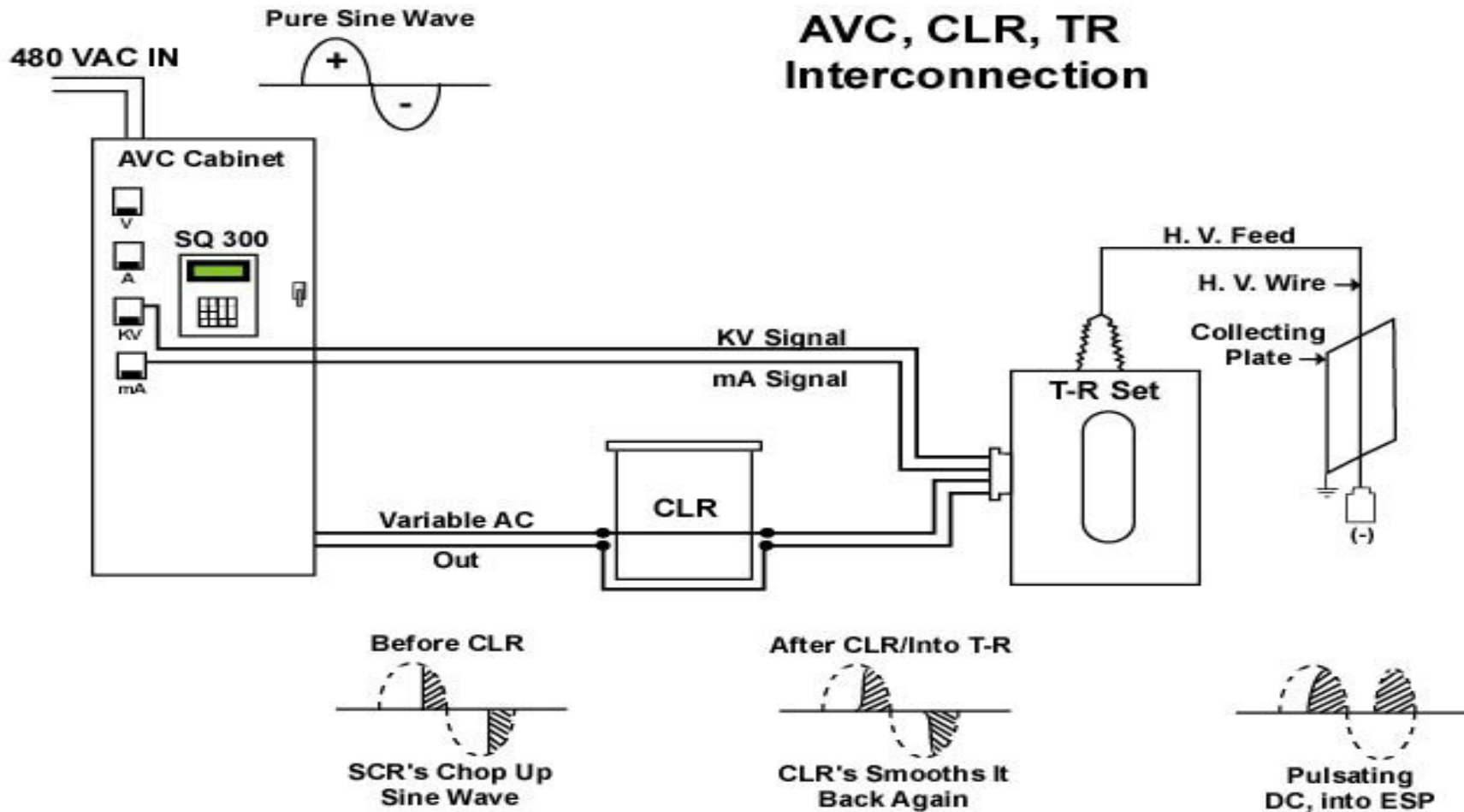



# AVC Spark Response

steag

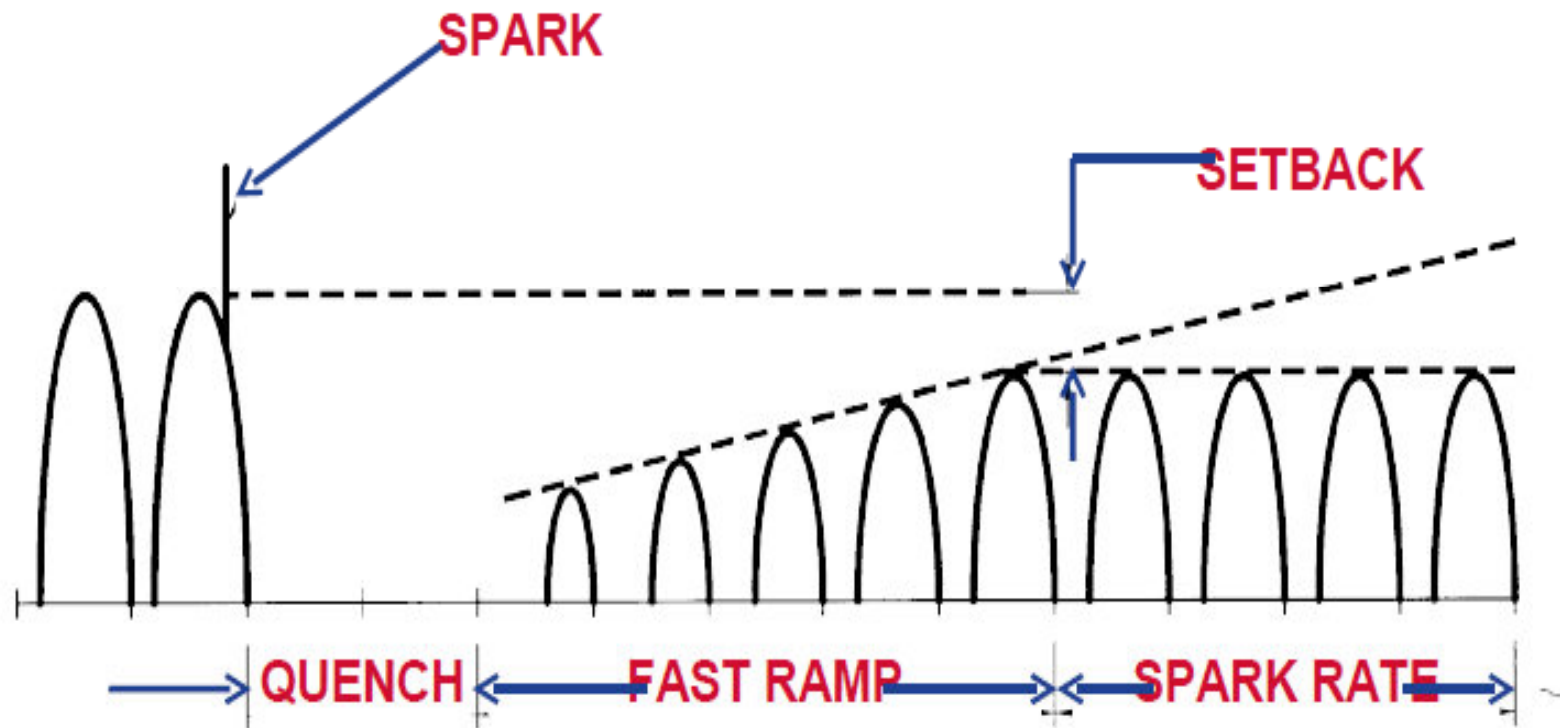


## Good Initial Settings for an AVC


steag

- 1. Quench = 1 Full Cycle**
- 2. Fast Ramp = 5 or 6 Half Cycles**
- 3. Setback = 15 to 20%**
- 4. Spark Rate = 30SPM**


# Proper AVC Response to Sparking

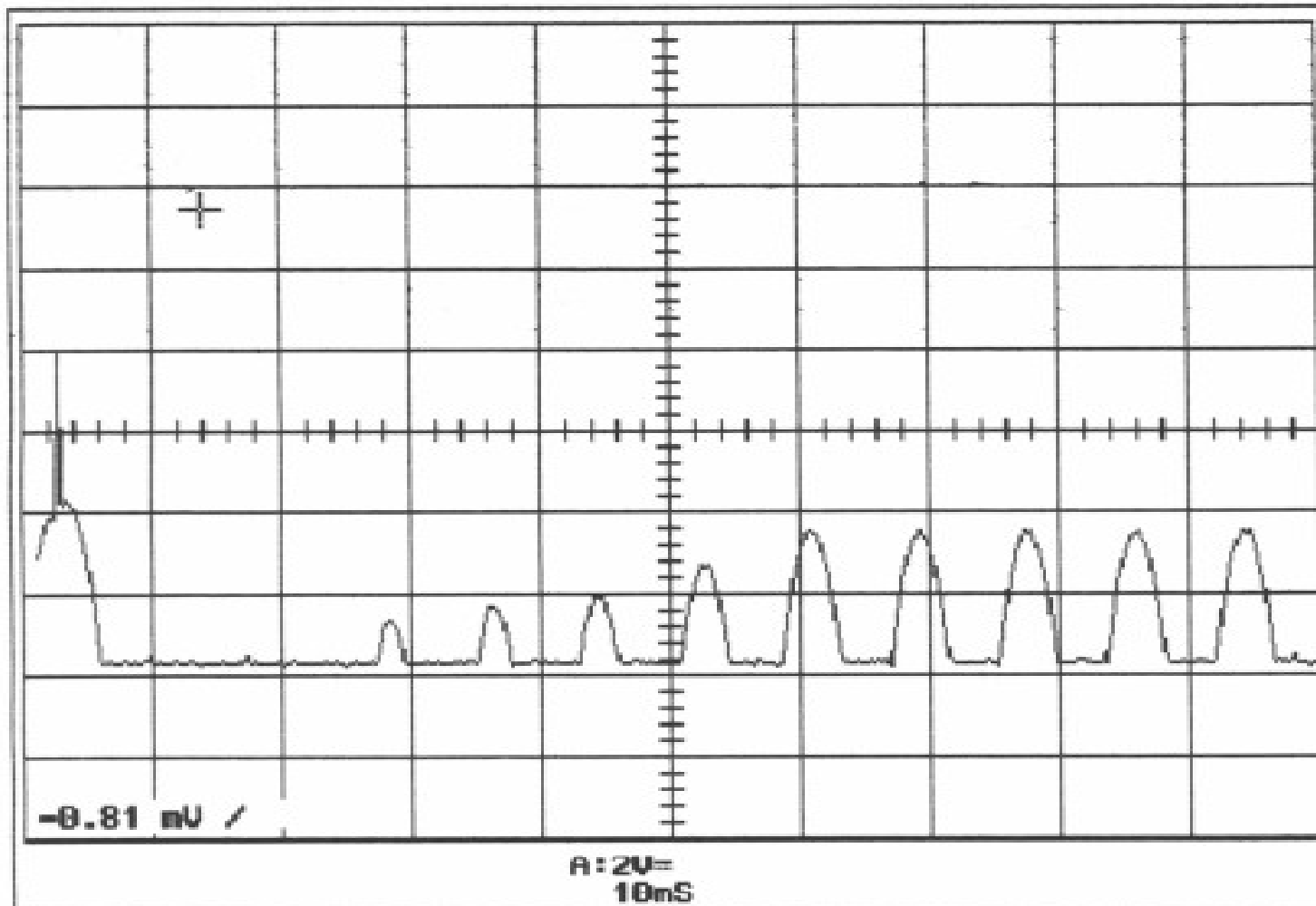

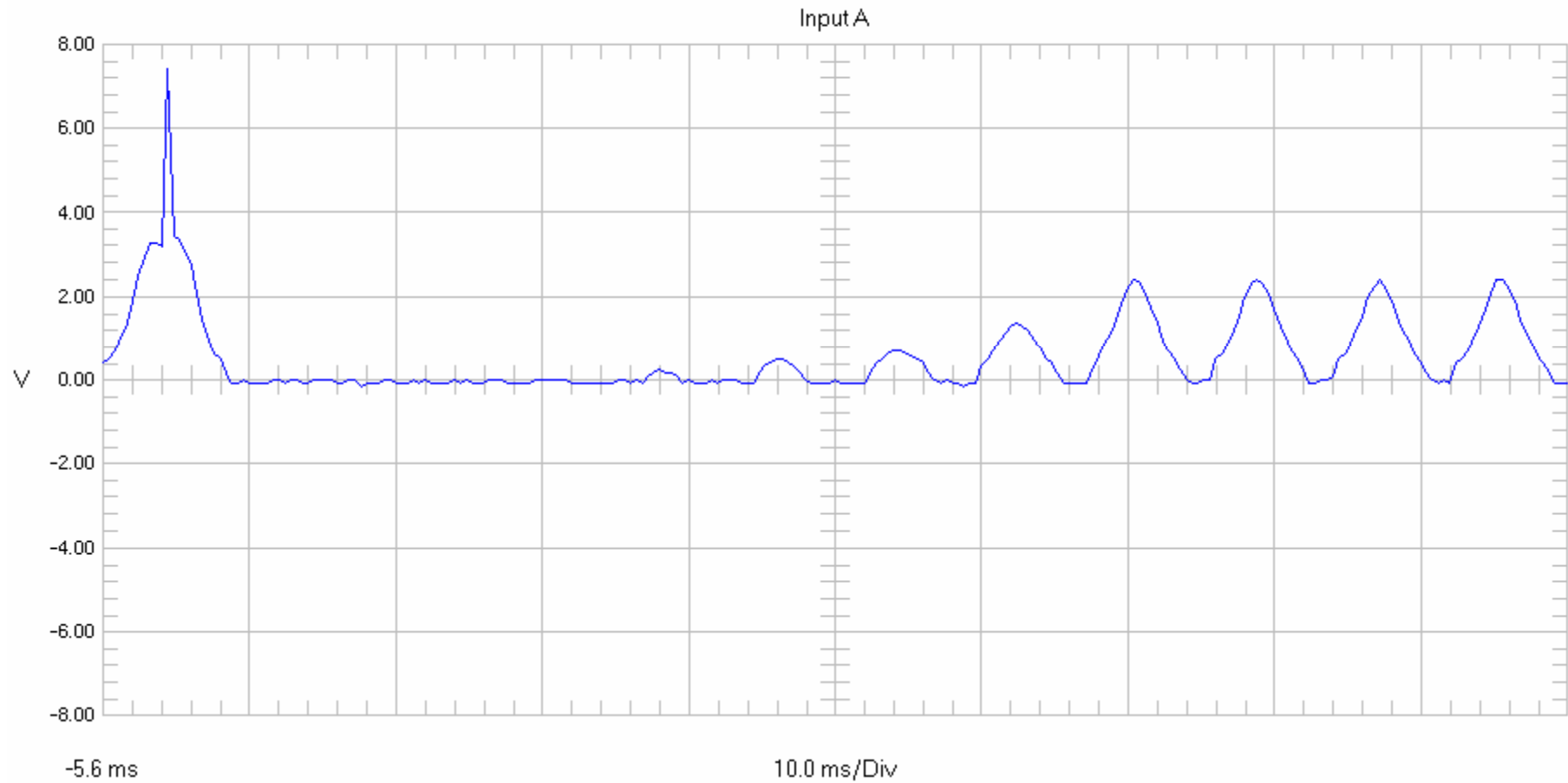
# Spark Response - Secondary Current Waveform


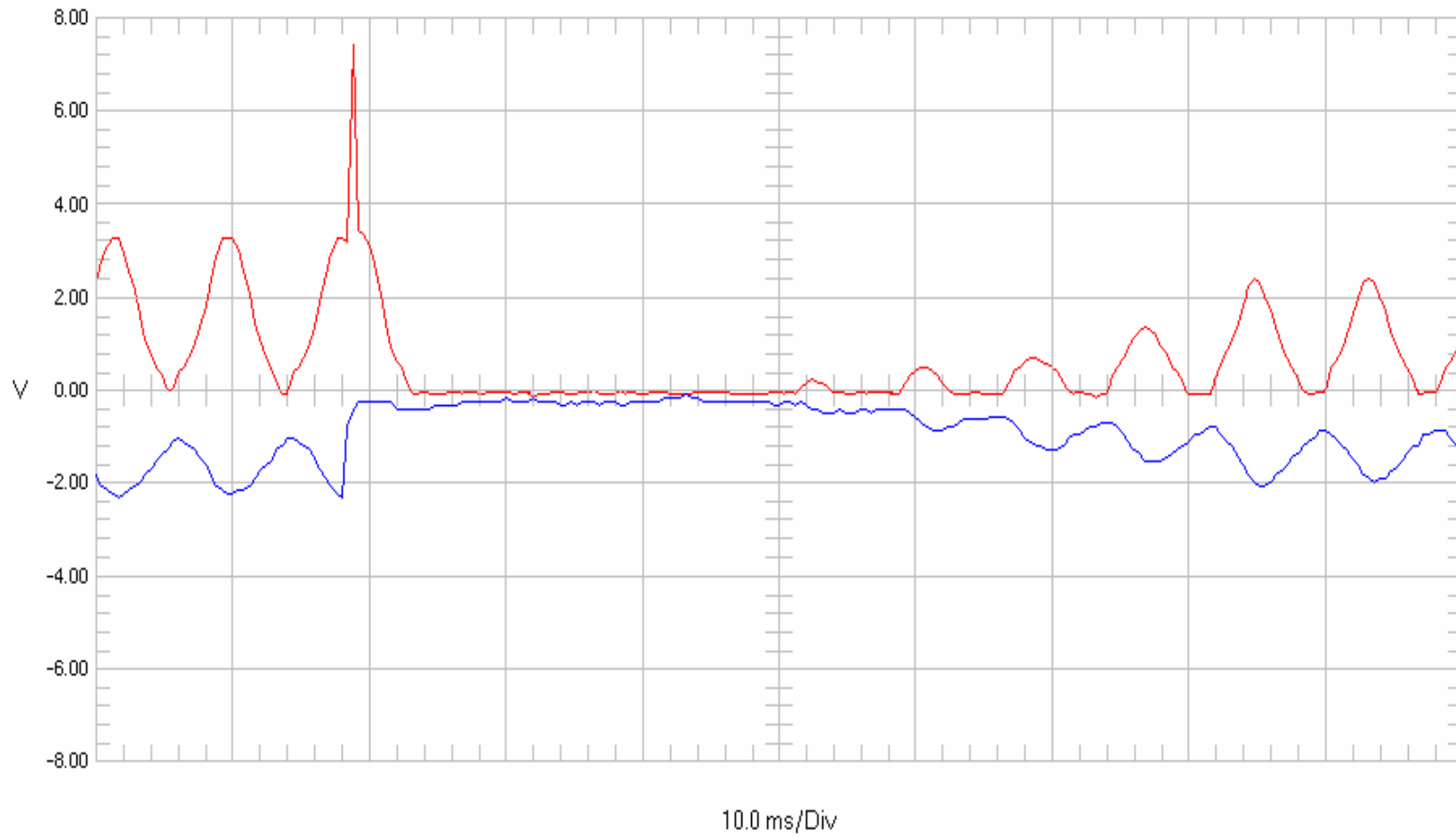
# Spark Response - Secondary Current and Voltage Waveforms




## Typical Spark Response - mA & KV

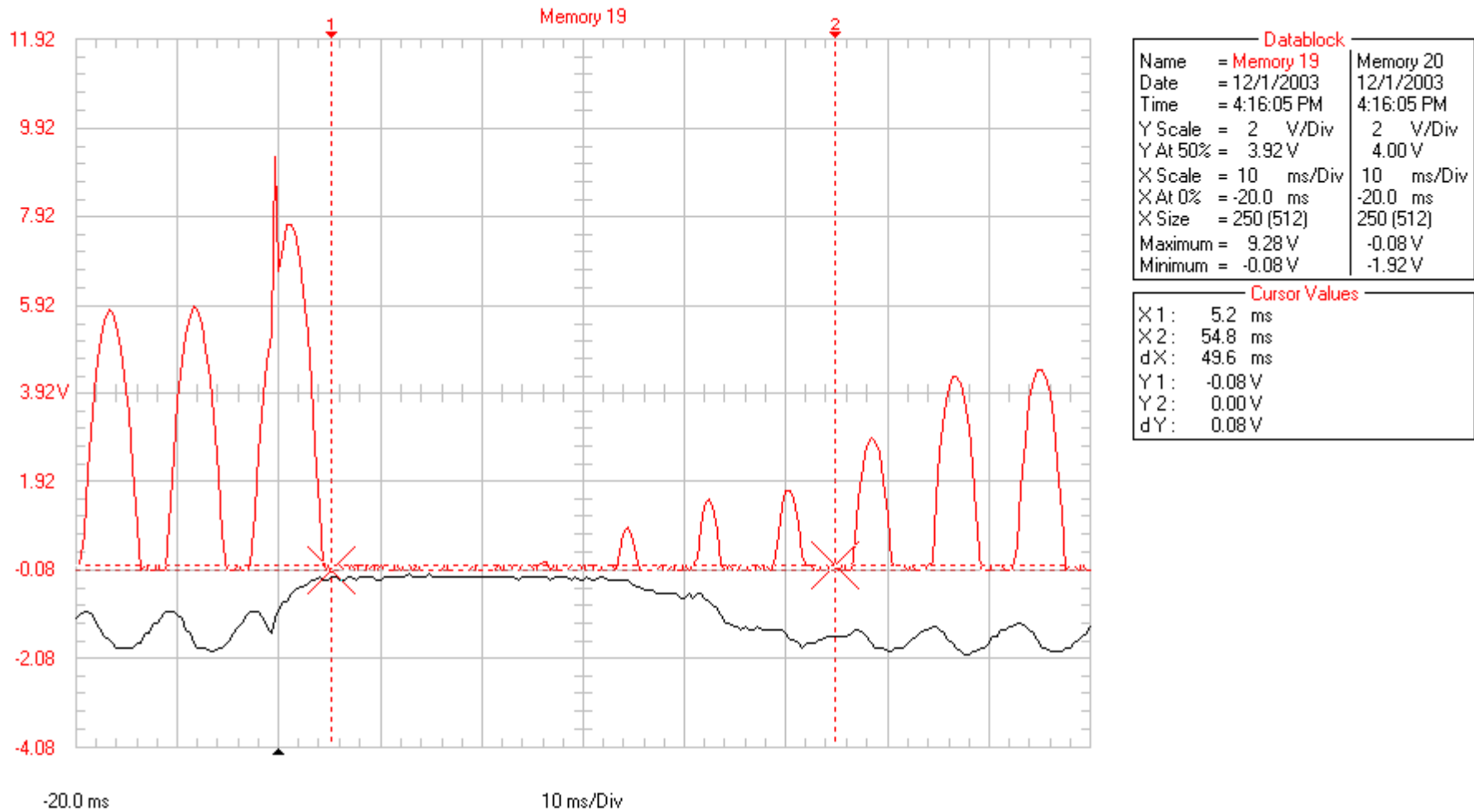


9&10F mA/KV

# Further Control – A Search Ramp Rate

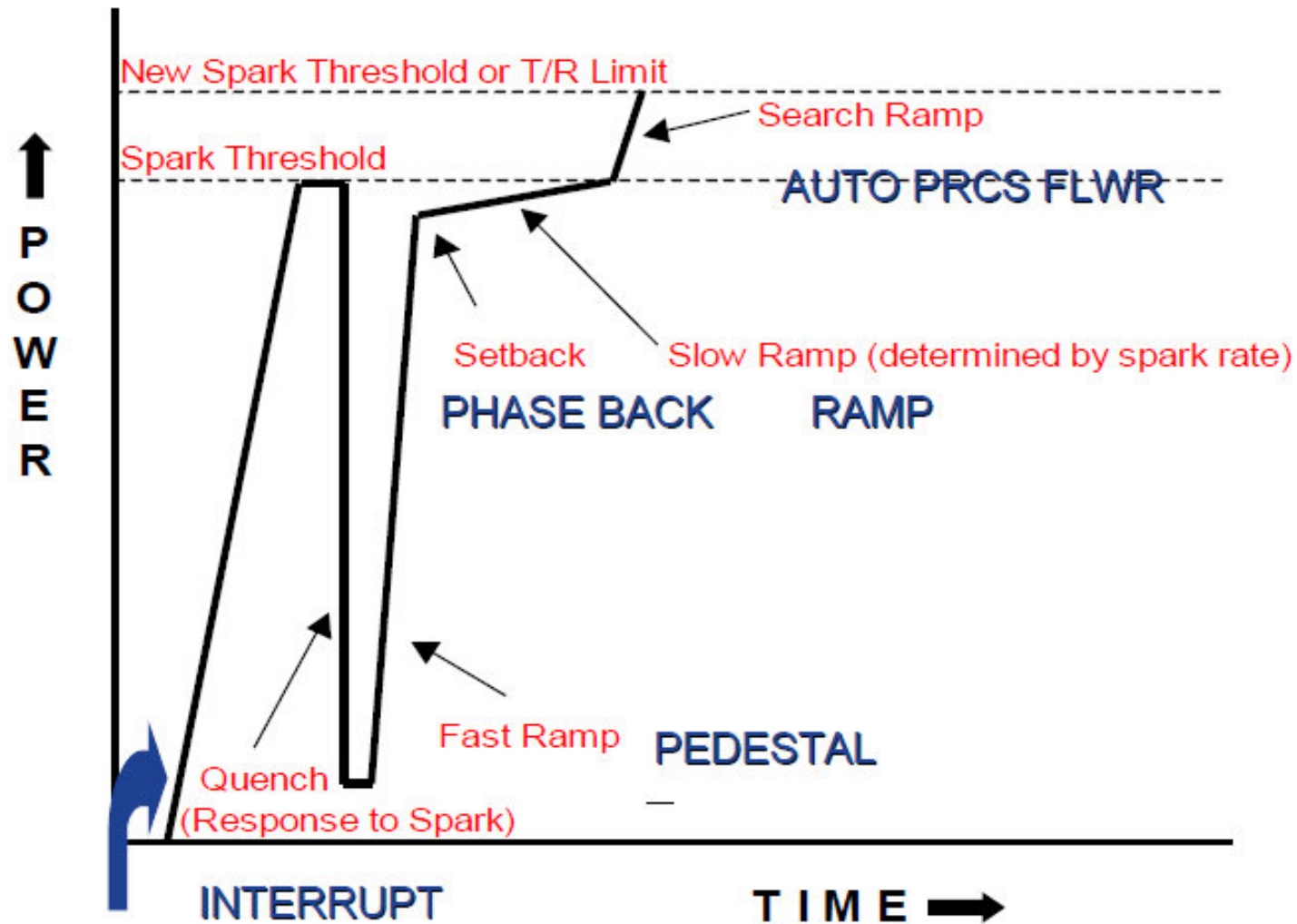


# Spit Spark Response (mA) Ramp Rate

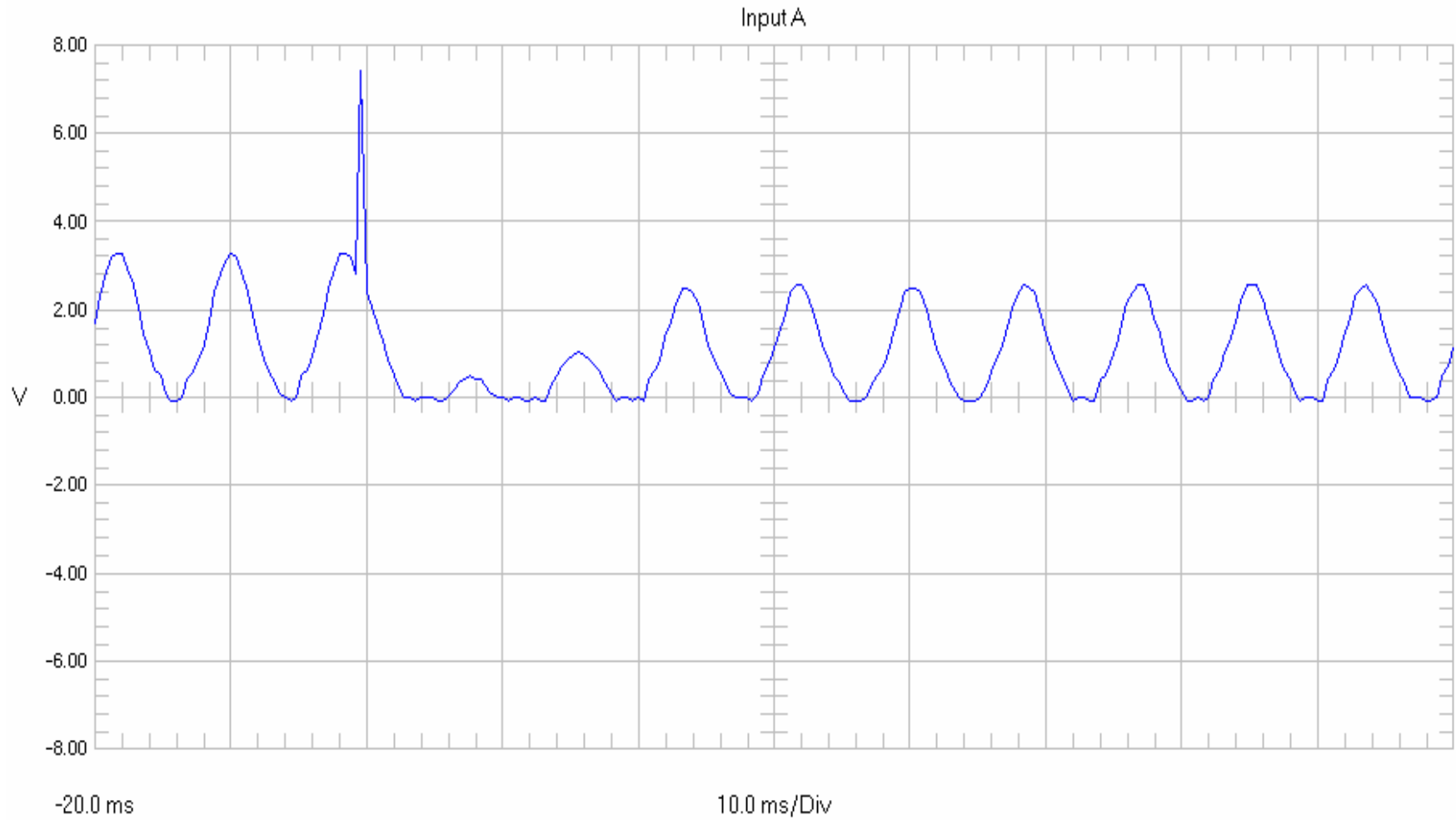


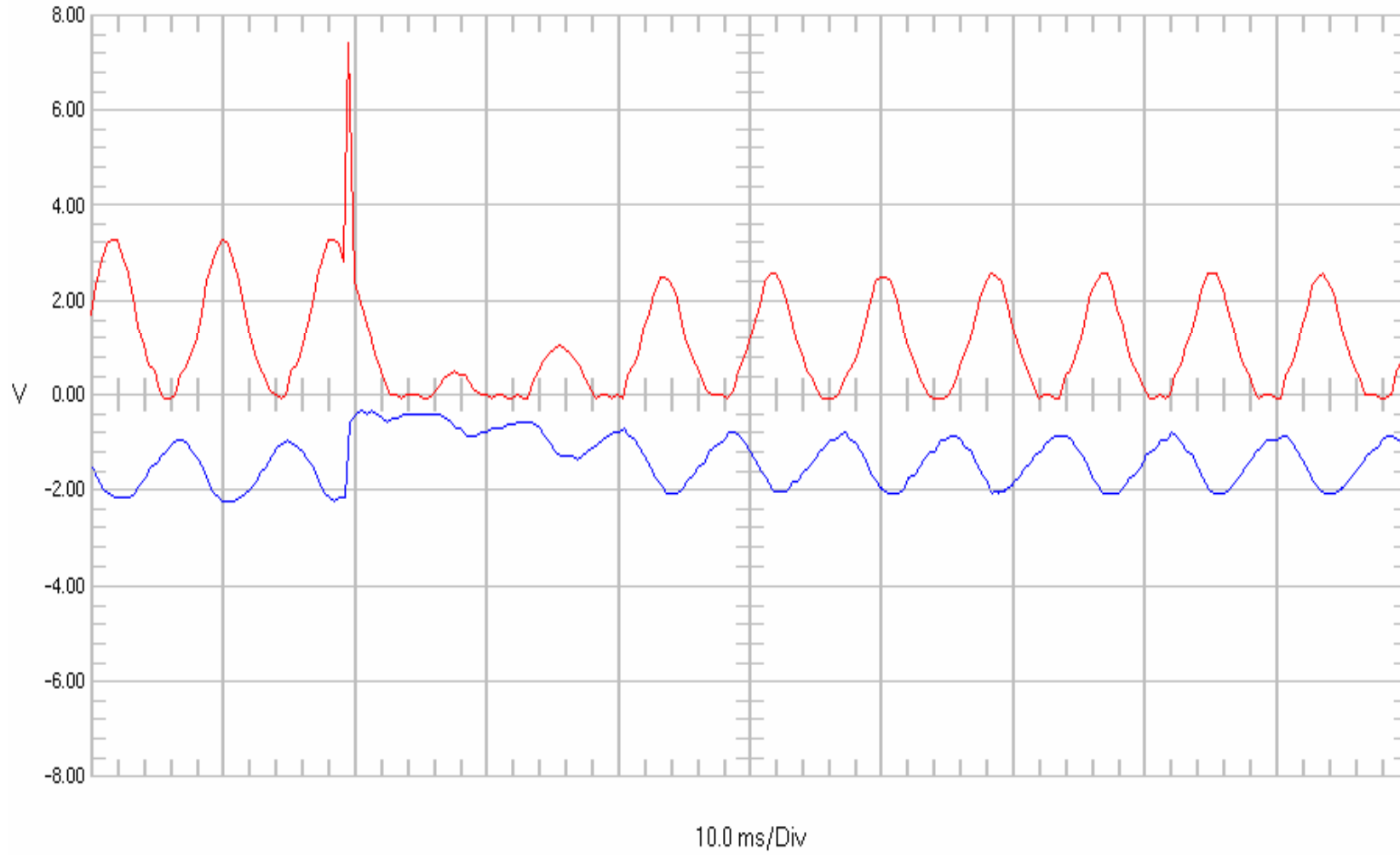
# Spit Spark Response - Secondary Current and Voltage Waveforms



## Examples of AVC 's at a Limit

# AVC SPARK LIMITED – DOING IT'S JOB

steag




# T/R Current Limited with Sparking

steag



# T-R CURRENT LIMITED WITHOUT SPARKING

steag

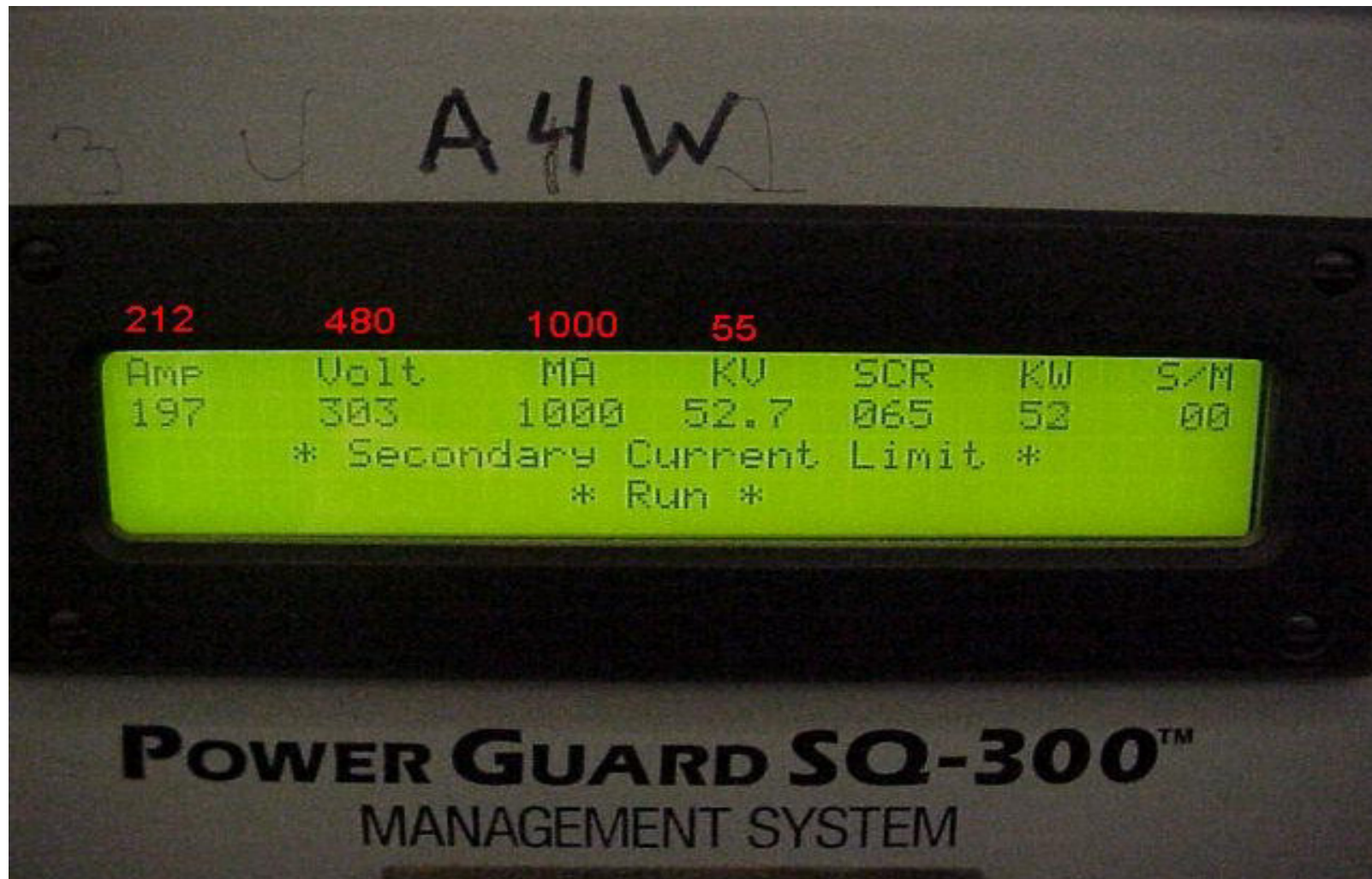

# T-R VOLTAGE LIMITED WITH SPARKING


steag



## What is meant by “Healthy Limits?”

- Primary or Secondary Limit is not healthy when accompanied by a Primary Voltage level  $< 90$  VAC or a Secondary level  $< 12$  KV. It usually indicates a short circuit.
- Secondary Voltage Limit is not healthy when there is very little Secondary Current. It usually indicates an open circuit.
- Neither condition is aiding in particle capture

# The T-R Set

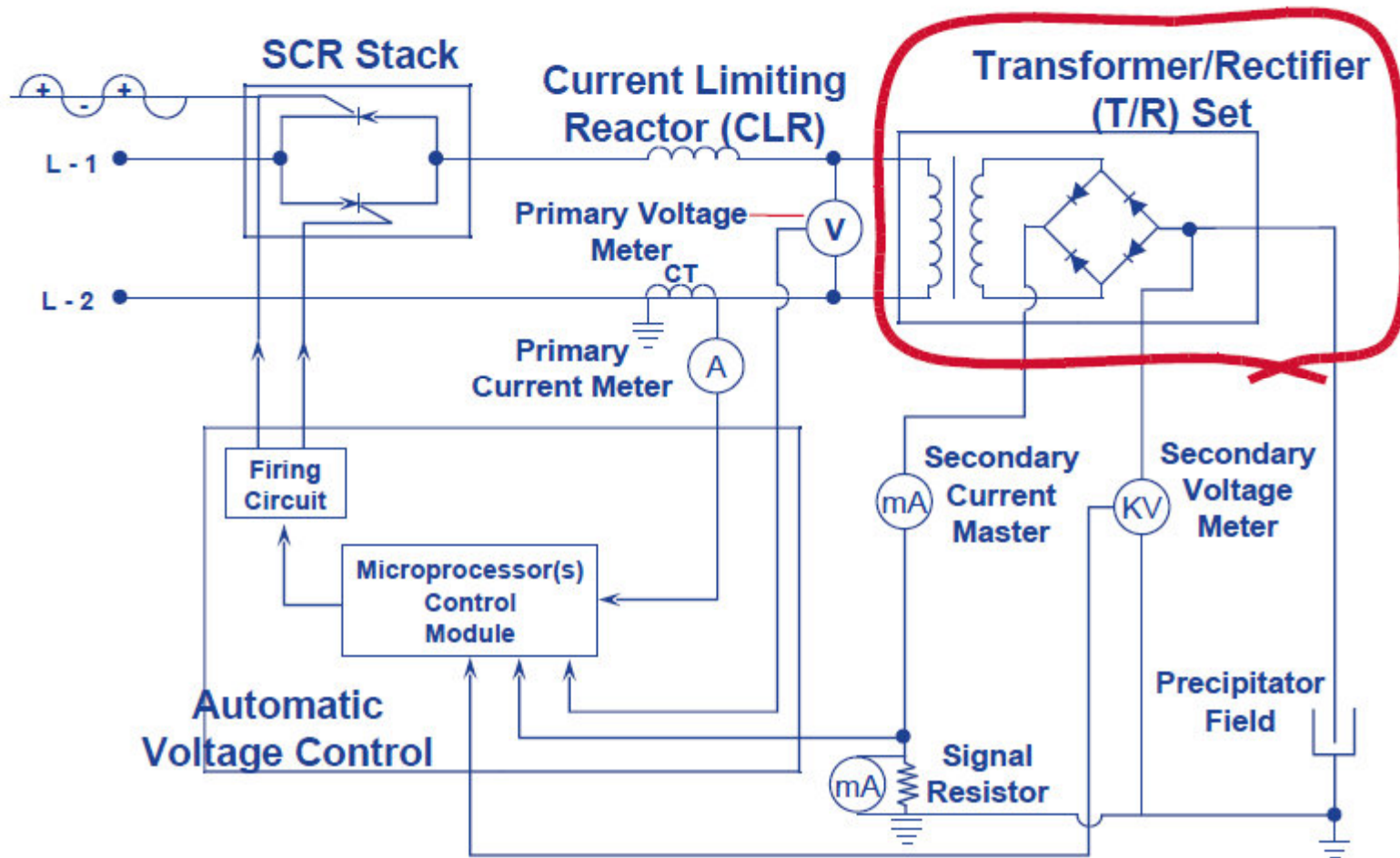



# Transformer Rectifier (T/R) Set

steag



# Inside T/R Tank

steag



# High Voltage Transformer

steag



# Diode Stack

steag




# T/R Set -Low Voltage Junction Box

steag



# Low Voltage Junction Box


steag

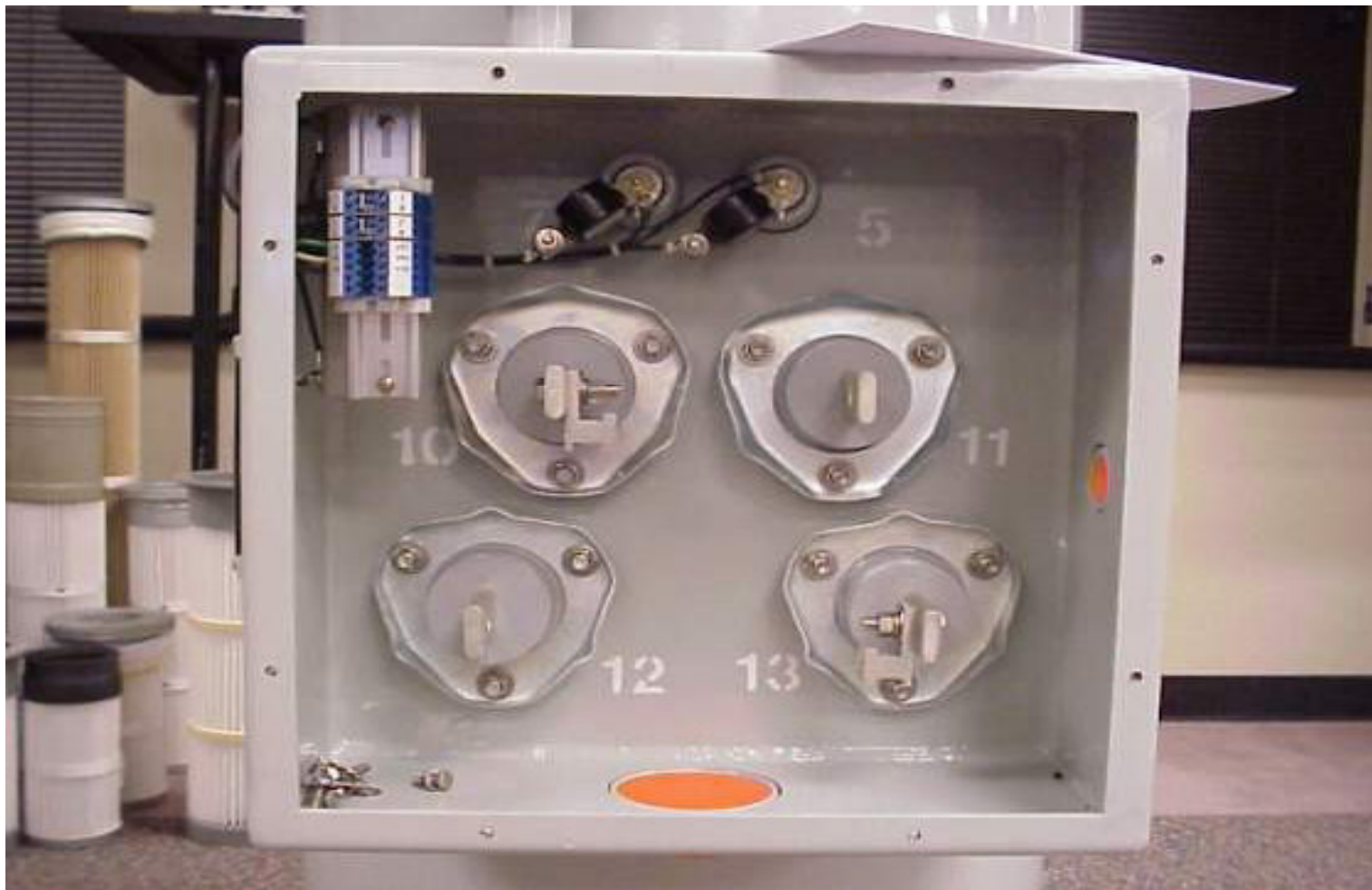

# T/R Nameplate




# The KV Meter

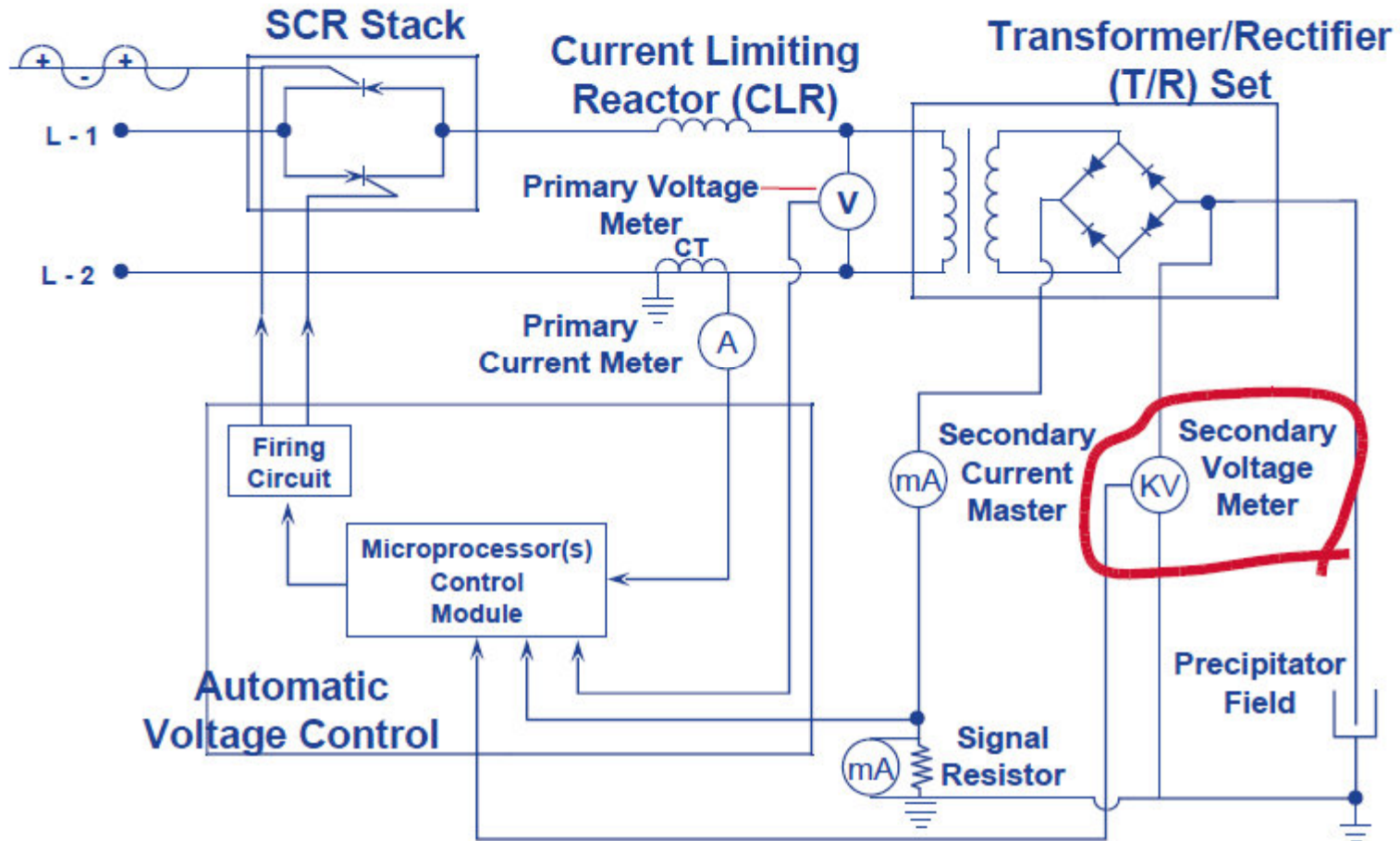




# Voltage Divider

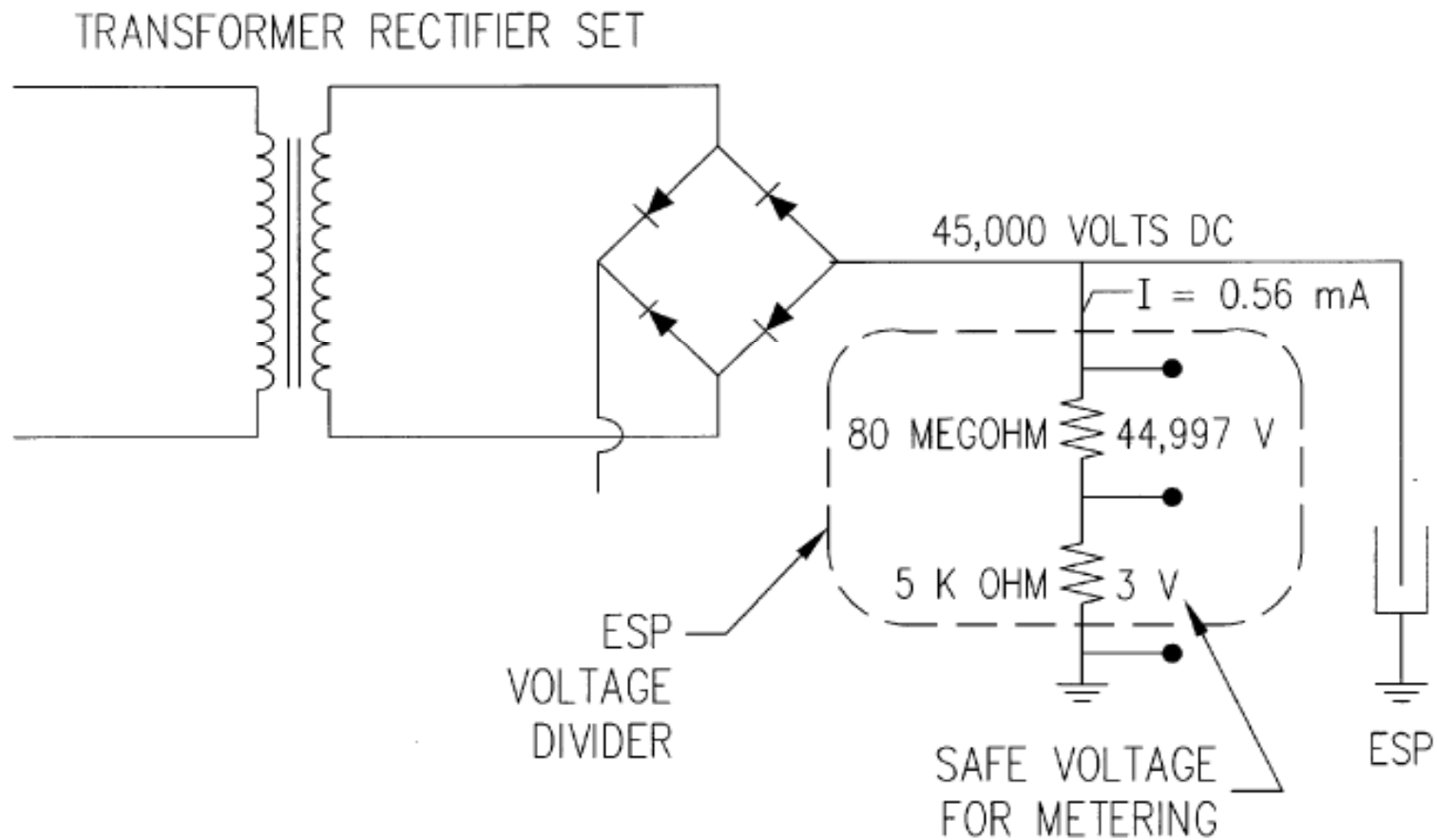


# SCR'S

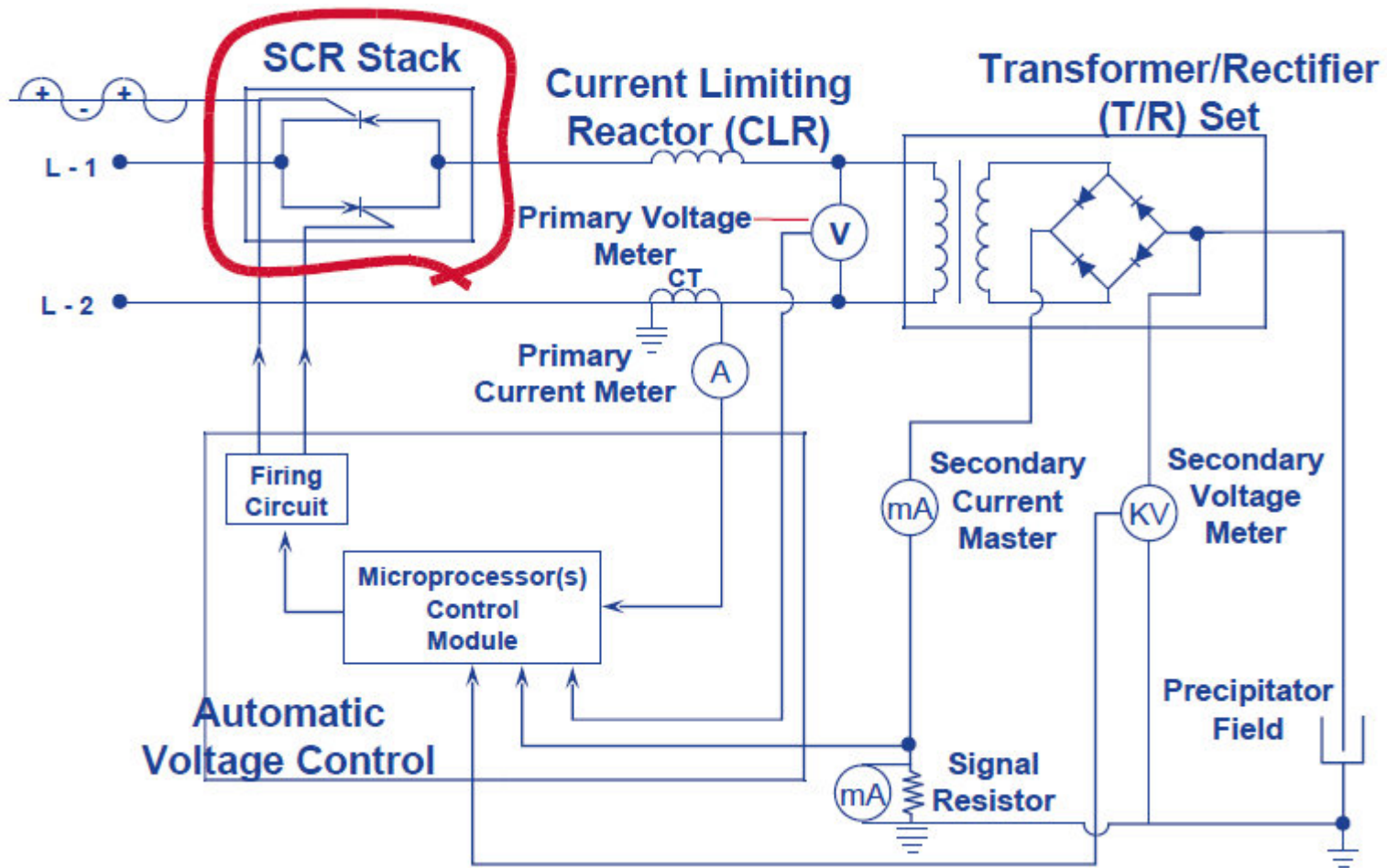


SCR

steag

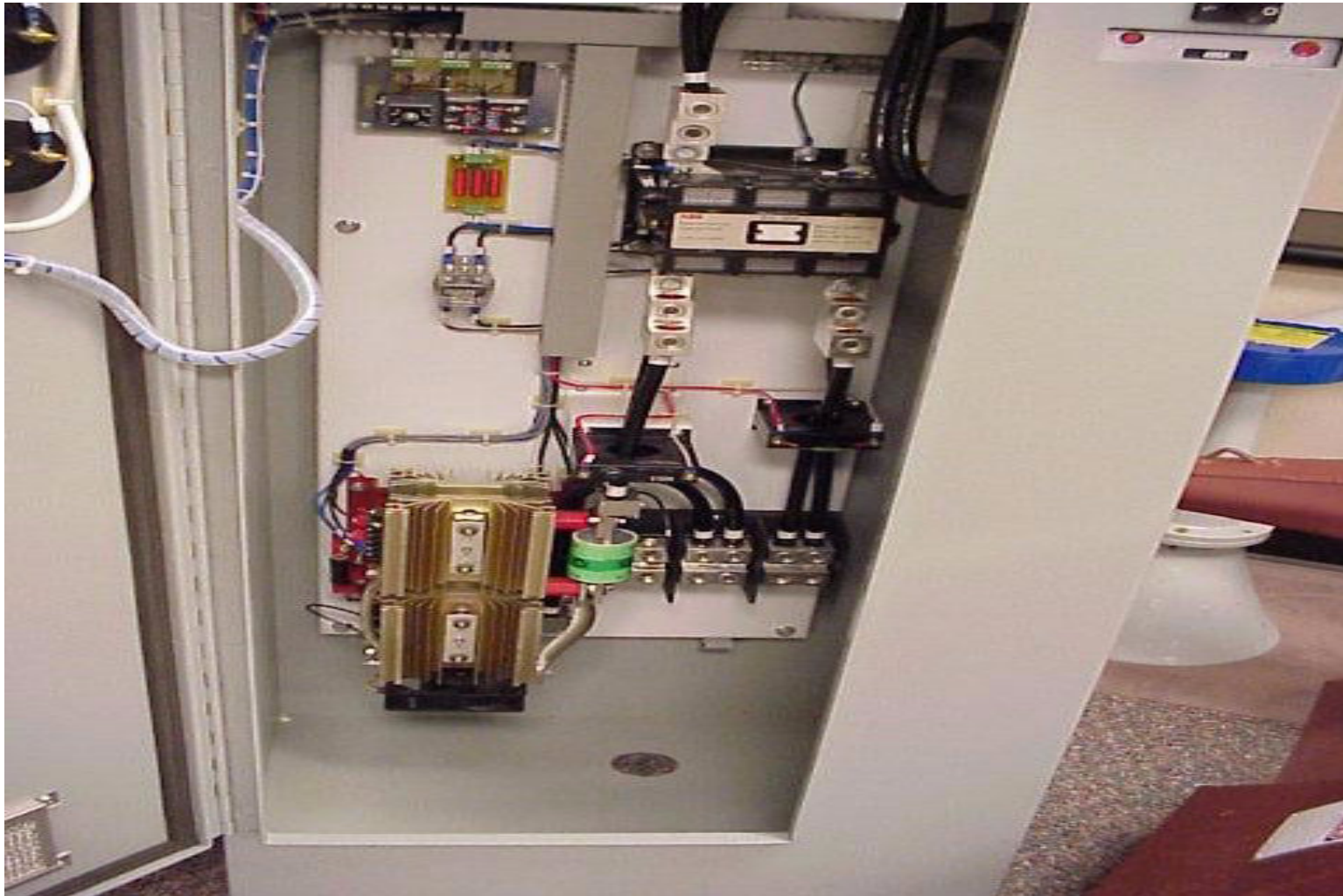


# Typical Sine Wave

steag

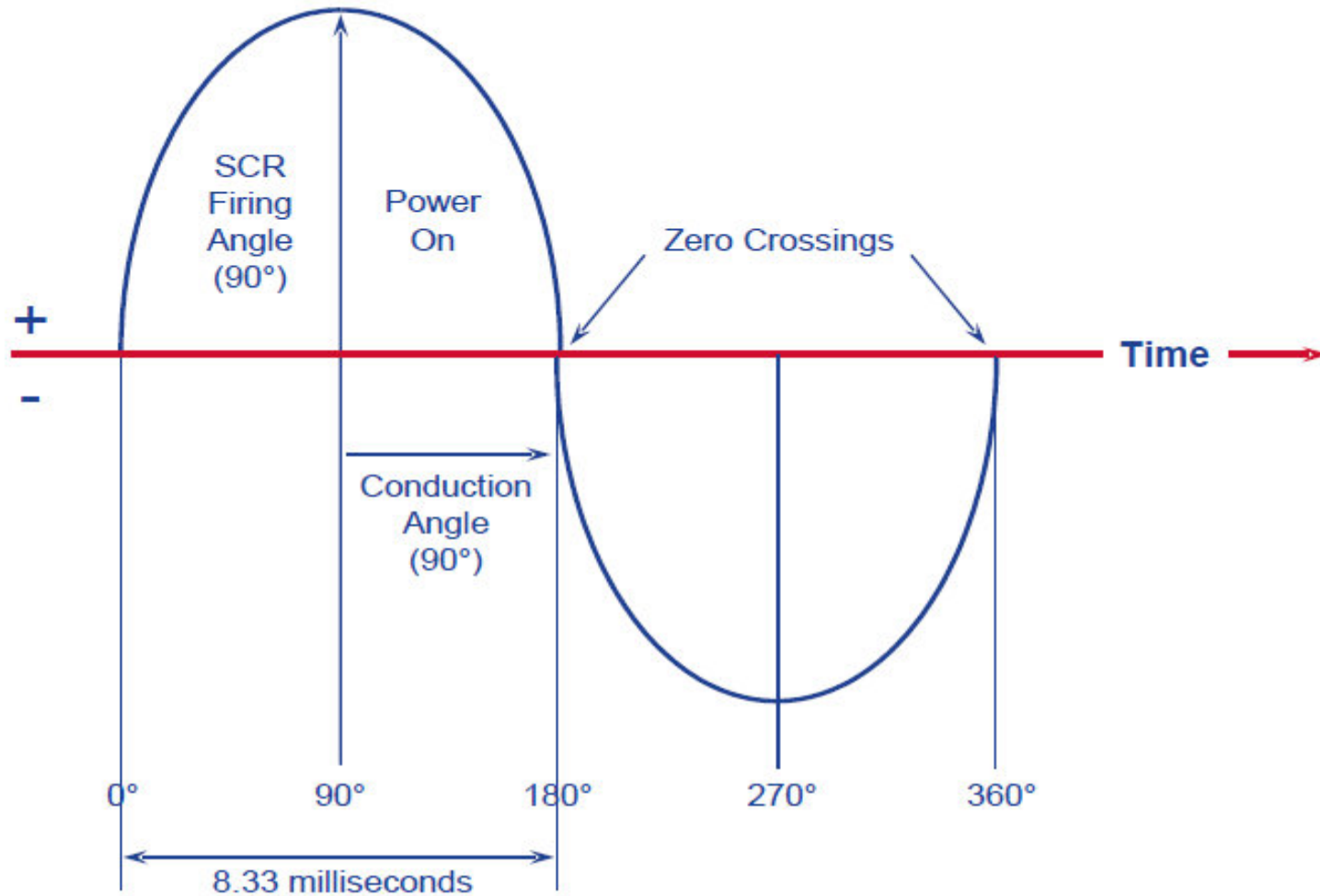

## SCR: Low Voltage to T-R Set


steag

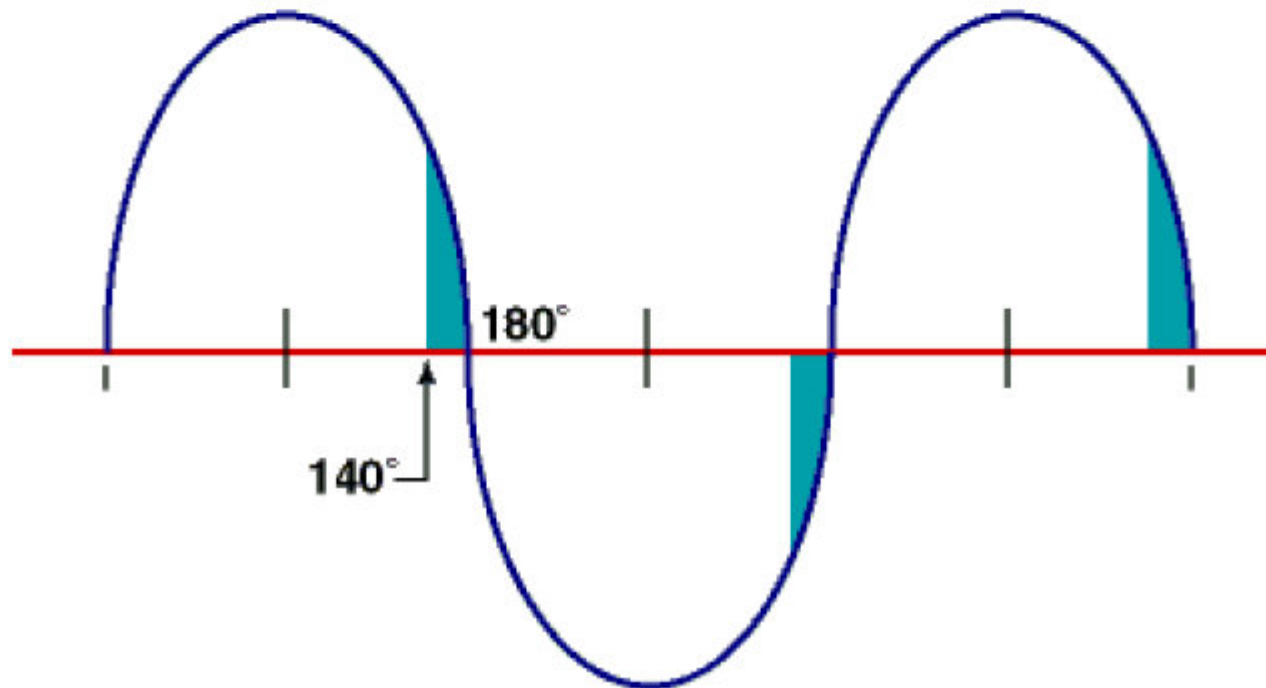

Firing Angle  $140^\circ$   
Conduction angle  $40^\circ$

# SCR: High Power to T-R Set


steag

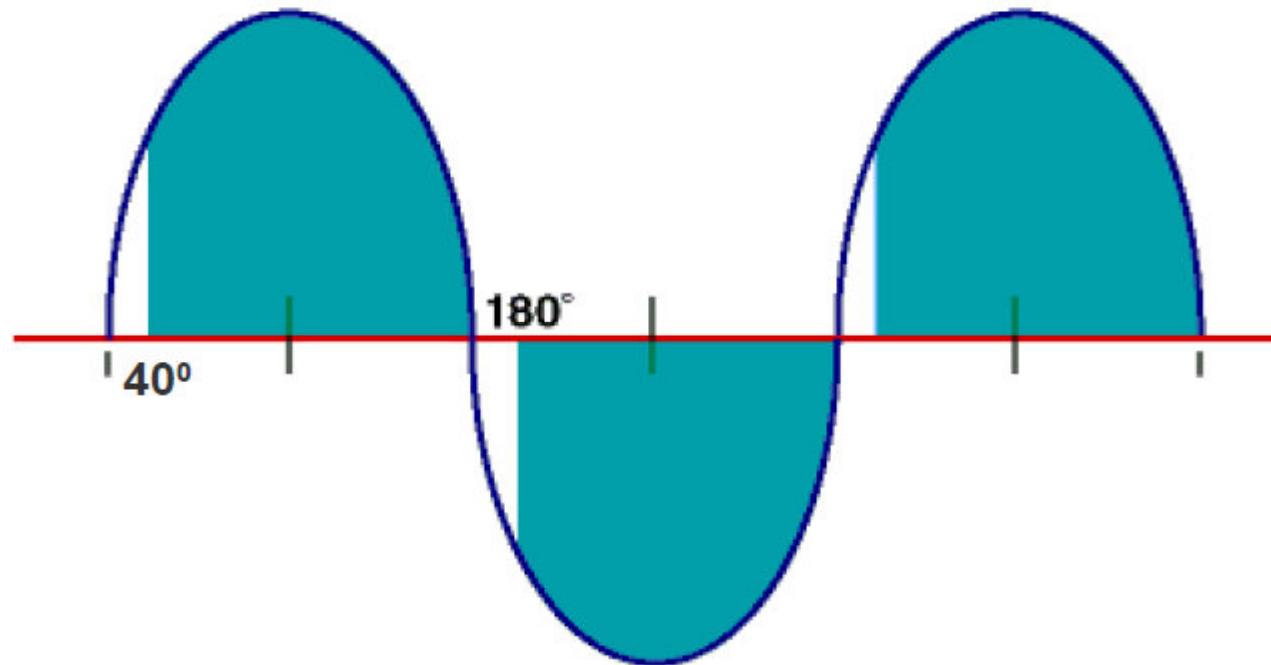

Firing Angle  $40^\circ$   
Conduction angle  $140^\circ$


# The CLR

**steag**

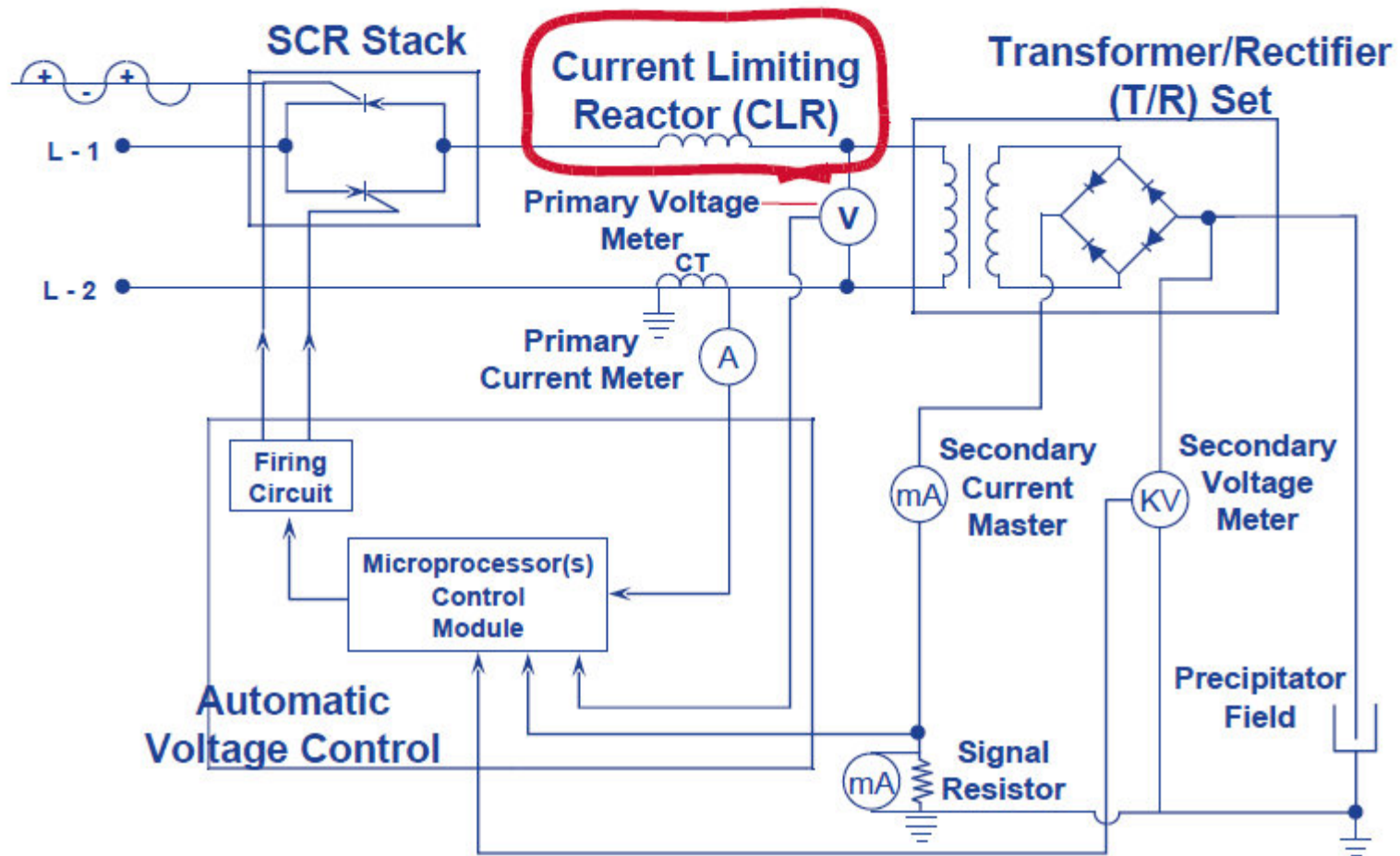

# Current Limiting Reactor (CLR)


steag

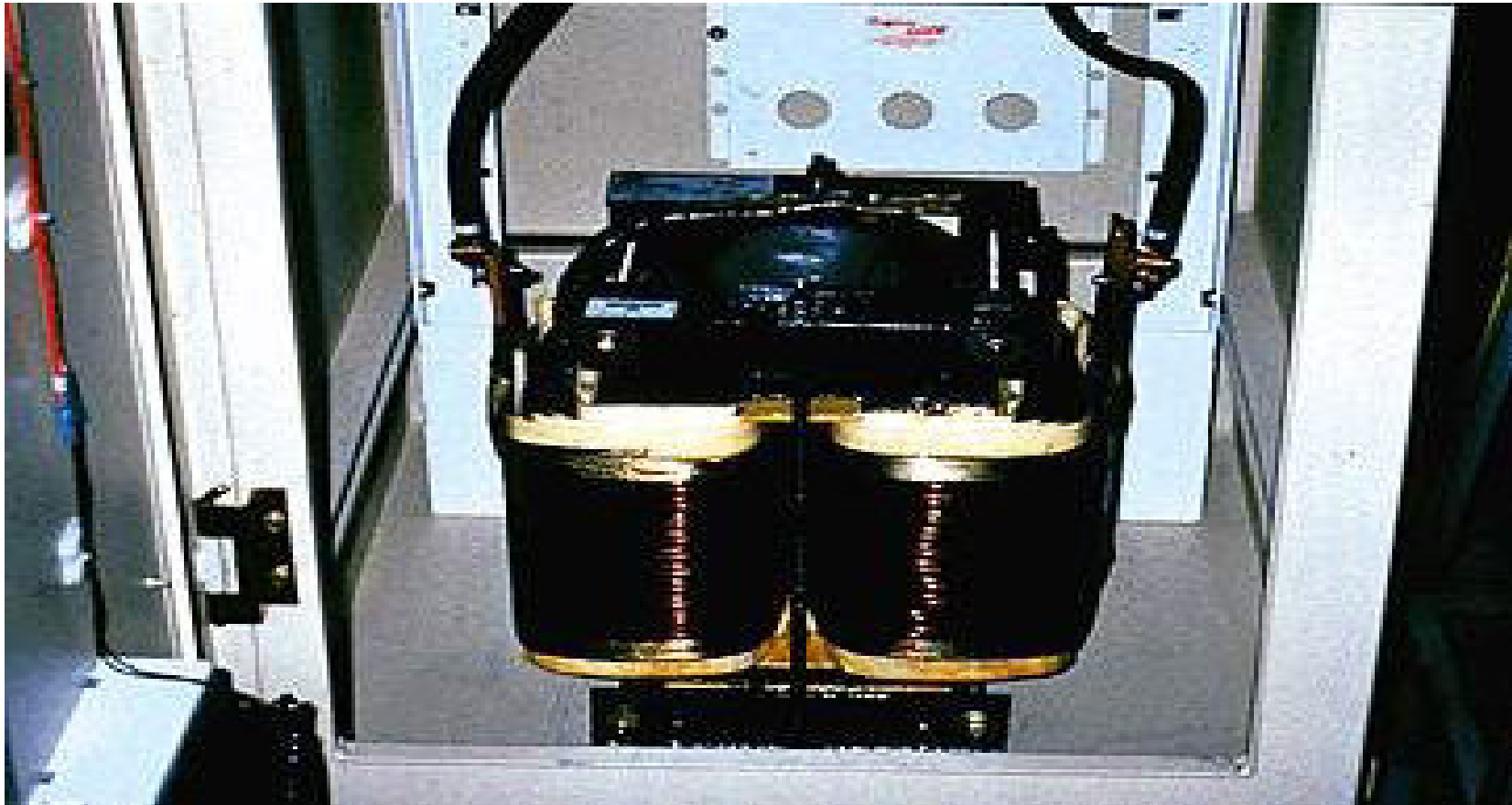



# Current Limiting Reactor

steag

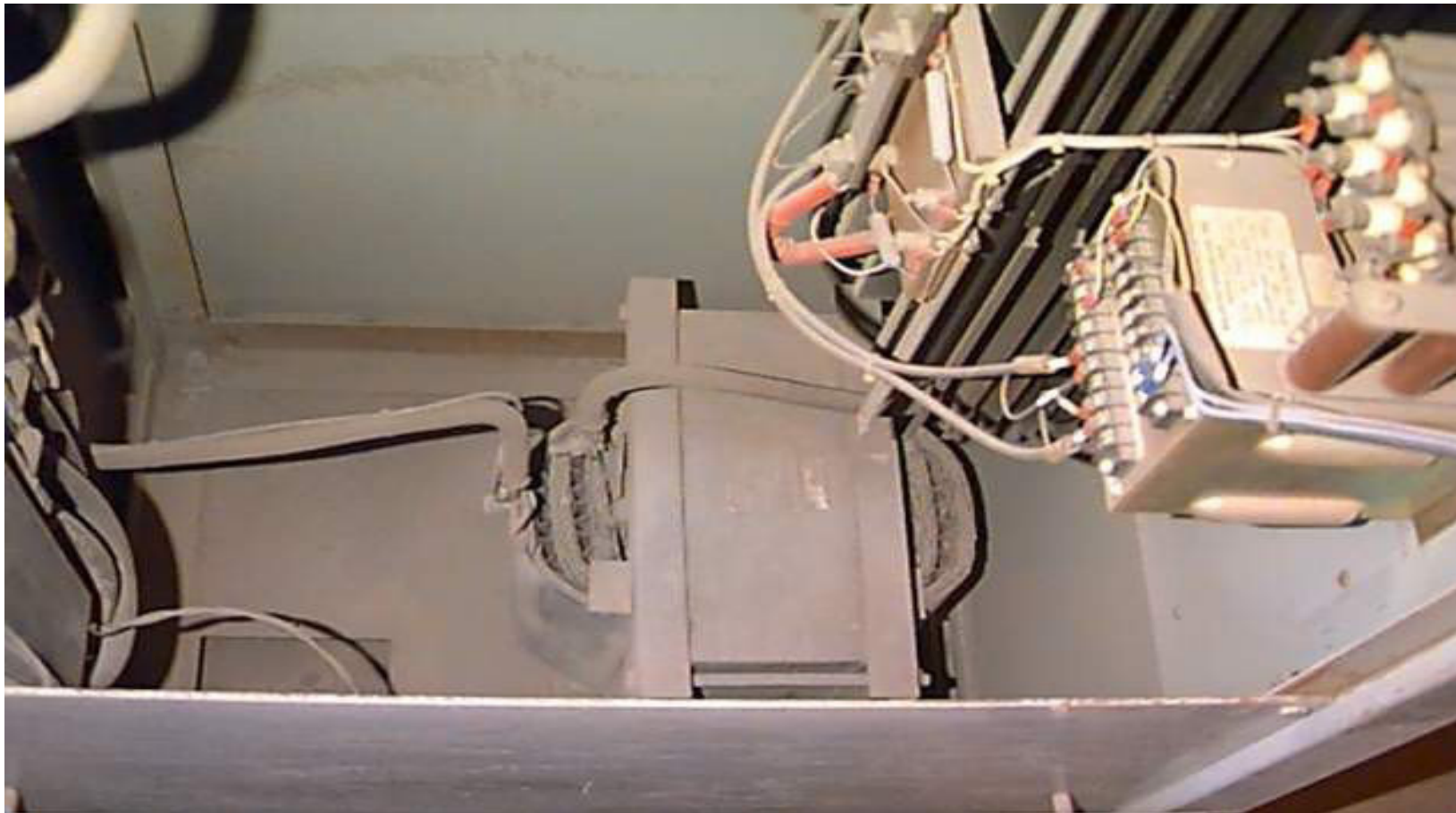

# Current Limiting Reactor at T-R Set


steag


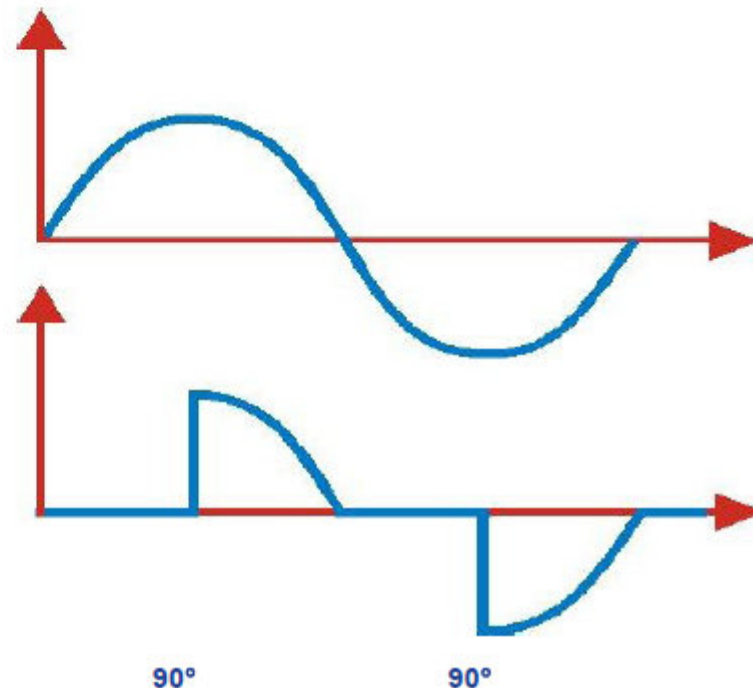
# SCR's are why CLR's are Needed


steag

- The diagram would represent the waveform with the SCRs turning on at  $90^\circ$ .
- If this waveform were applied to the T/R set, very inefficient operation would occur.
- Output power from the T/R set would be greatly reduced.


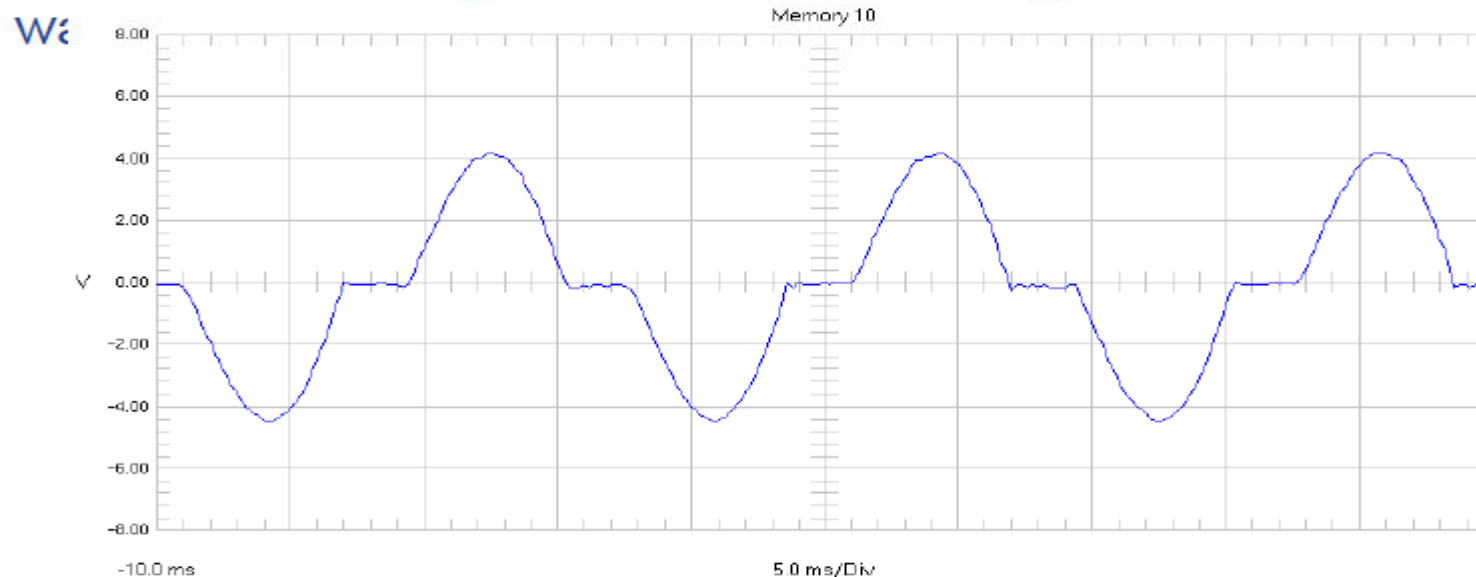
# Electrical Basics: CLR

To increase the efficiency of the T/R set, a device called a CLR (current limiting reactor) is used. A CLR is an inductor. Recall that the property of an inductor is to oppose a change in current. Because of this property, the shape of the current waveform is changed and it starts looking more like a sine




# CLR Function



- **Limit short circuit current**
- **Shape T/R secondary wave to be more Sinusoidal**
- **Provide proper form factor**
- **Protect SCRs and T/R diodes from steep current rise**
- **Increase precipitator voltage and current**
- **Not to be confused with air core reactor**

# CLR – Waveform Changes with Impedance

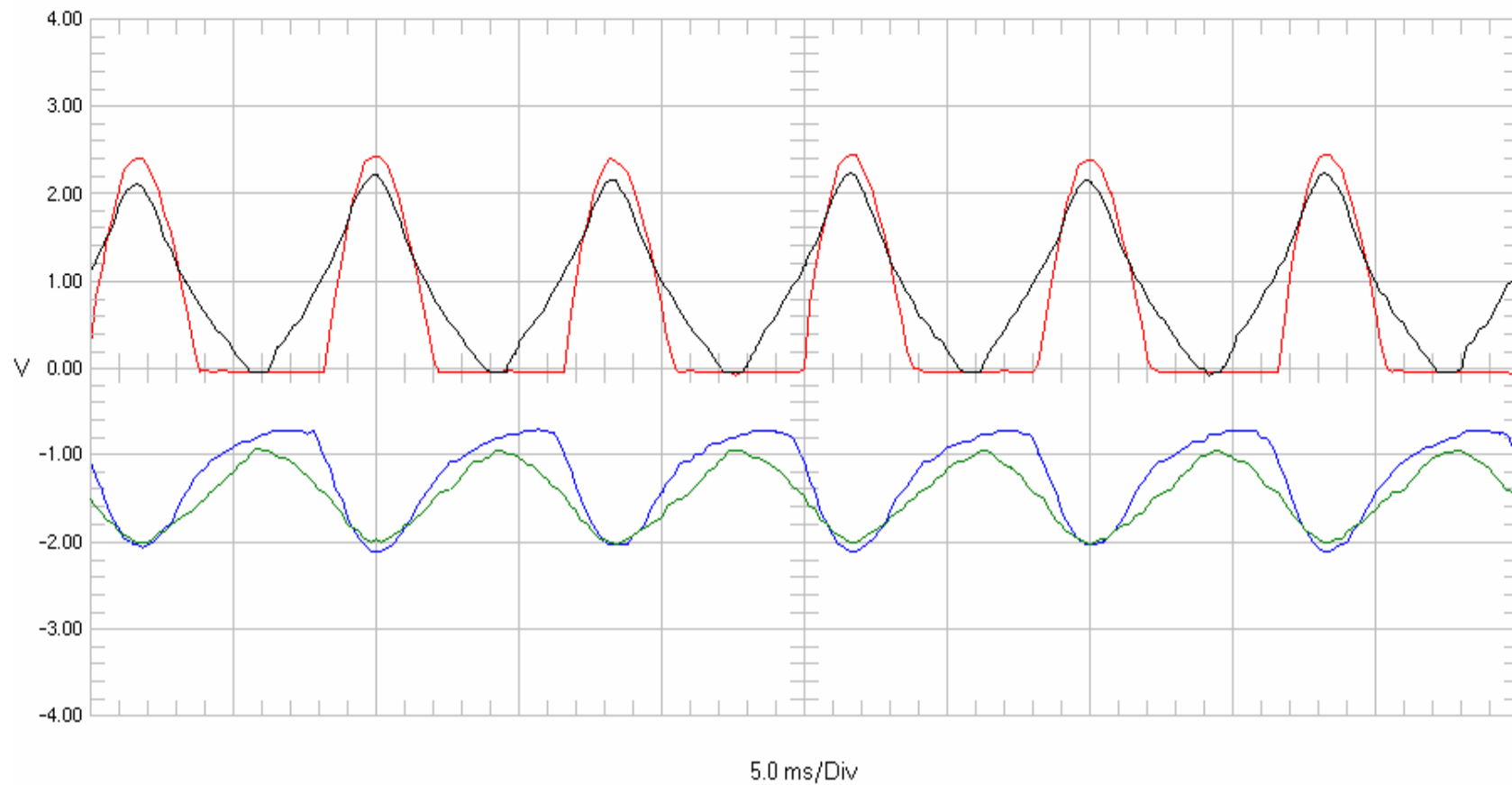

# Proper CLR Sizes for Common T/R Sets



All T/R primaries are rated at 400V

PRI Current (Amps)	Sec. Current (mA)	Minimum (mH)
40	250	13.0
80	500	6.6
120	750	4.4
160	1000	3.3
200	1250	2.6
240	1500	2.2

# Basic Troubleshooting

**steag**





## TR Nameplate Values (For this exercise)

steag

Primary Current	160 Amps
Primary Voltage	480 Volts
Secondary Current	1200 mA
Secondary Voltage	45 kV

First Indication

```
160 480 1200 45  
AMP Volt MA KV SCR KW S/M  
160 045 1067 00.9 081 00 00  
* Primary Current Limit *  
* Run *
```

Second Indication

```
AMP Volt MA KV SCR KW S/M  
160 045 1067 00.9 081 00 00  
* Primary Under Voltage Alarm *  
* Main Power Off *
```

# Short

# Close Clearance

steag

160

480

1200

45

AMP	Volt	MA	KV	SCR	KW	S/M
009	110	0027	14.0	170	04	30
* Spark *						
* Run *						

# Conductive Dust, Outlet Field

steag

160	480	1200	45			
Amp	Volt	MA	KV	SCR	KW	S/M
160	382	1177	32.1	081	38	00
* Primary Current Limit *						
* Run *						

# Bad KV Return



160	480	1200	45			
Amp	Volt	MA	KV	SCR	KW	S/M
160	382	1177	00.2	083	00	00
* Secondary Under Voltage Alarm *						
* Main Power Off *						

Open

steag

160

480

1200

45

AMP	Volt	MA	KV	SCR	KW	S/M
000	452	0000	45.0	050	00	00
* Secondary Voltage Limit *						
* Run *						

# Normal Running Condition

steag

160      480      1200      45

Amp	Volt	MA	KV	SCR	KW	S/M
100	239	0584	29.9	100	17	30
		* Spark *				
		* Run *				

# SCRs Not Firing

steag

160

480

1200

45

```
Amp      Volt      MA      KV      SCR      KW      S/M
000      000      0000    00.0    016      00      00
* SCR Firing Angle Limit *
* Run *
```



Thank You.

**stead**